

circuit is 80W. Determine the values of resistor and capacitor.

UNIT-II

Fig 2

4. a) Derive the formula for the resonant frequency of a series RLC circuit. 7M

OR

b) A series circuit having a resistance and a capacitance draws a current of 2.4A from a 100V, 50Hz, single phase ac supply. The power consumed in the

10 V


3. a) Define and determine the Average and RMS values of a sinusoidal voltage.

b) Two impedances $Z_1 = (8 + j6)$ ohm and $Z_2 = (4 - jX_c)$ ohm are connected in parallel. Find the value of X_c such that the circuit resonates. 7M

5. State and explain Norton's theorem with an example.

OR

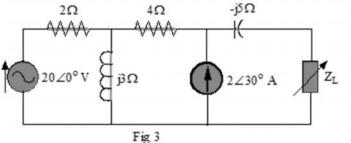6. In the circuit of fig 3, determine the impedance to be connected across the load terminals for maximum power transfer if the load consists of a resistance in series with a reactance. Also, find the value of the maximum power transferred.



14M

14M

7M

7M

14M


7M

7M

14M

UNIT–IV

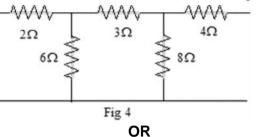- 7. a) Define the hybrid parameters of a 2 port network.
 - b) Determine the Z parameters of the network shown in fig 4.




8. Two, 2 port networks are connected in parallel. The Z parameters of the networks are given below:

 $Z_{A} = \begin{bmatrix} 11 & 3\\ 4 & 5 \end{bmatrix} \text{ and } Z_{B} = \begin{bmatrix} 2 & 1\\ 1 & 2 \end{bmatrix}$

Determine the Y parameters of the parallel combination.

UNIT–V

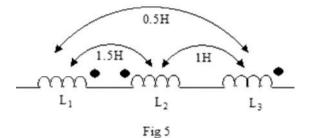9. a) Three inductances $L_1 = 2H$, $L_2 = 1.8H$ and $L_3 = 2.6H$ are connected in series as shown in fig 5. Determine the equivalent inductance.




7M

7M

b) Deduce the equation for the coefficient of coupling when two coils are magnetically coupled.

OR

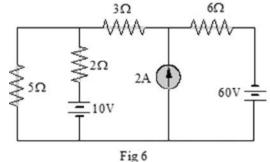10. a) For the circuit of fig 6, construct the graph of the network and obtain the tie set matrix.



7M

7M

b) Define the term dual networks. Elaborate the procedure of obtaining the dual of the given network.

ode:	100	et Number : R-14	
de:		.Tech. I Semester Supplementary Examinations Nov/Dec 2017	
		Electro Magnetic Fields	
		(Electrical and Electronics Engineering)	
		ks: 70 Time: 3 Hou r all five units by choosing one question from each unit (5 x 14 = 70 Marks) ********	irs
		UNIT–I	
1.	a)	Define electric field intensity? Derive the expression for electric flux density due to an array of point charges?	-
	b)	Four infinite uniform sheets of charge are locate as follows:	
		10 pC/m ² at y=7, -8 pC/m ² at y=3, 6 pC/m ² at y= -1, -18 pC/m ² at y= -4. Find 11 at origin.	-
		OR	
2.	a)	State different types of charge distributions and express each of them in terms of their charge densities.	į
	b)	Given the potential v=10/r ² sin Θ cos Θ volts. Find D at (2, /2, 0). Calculate the work done in moving a 10µC charge from A(1,30 ⁰ ,120 ⁰) to B(4,90 ⁰ ,60 ⁰) UNIT–II	9
3.	a)	Define electric dipole and dipole moment. Find potential at a point due to the dipole.	
0.	b)	Find the capacitance of a co-axial capacitor.	
	~)	OR	
4.	a)	Derive the expressions for equivalent capacitance when two dielectrics in a	
	.,	capacitor are placed such that the interface is (i) parallel (ii) normal to electric field intensity	
	b)	The radii of the two spheres differ by 4cm and the capacitance of the spherical condensers is 53.33pF. if the outer sphere is earthed, calculate the radii assuming air as dielectric.	
		UNIT-III	
5.		Deduce the expression for magnetic field intensity at a point due to a circular current carrying wire.	1
		OR	
6.		The conducting triangular loop in the figure carries a current of 10A. Find t_{int} t (0,0,5) due to side-1 of the loop.	
		(0, 2, 0)	
			1.

UNIT–IV 7. Prove that torque experienced by a current loop placed in a uniform magnetic field is normal to the plane containing the magnetic dipole moment and magnetic flux density 14M OR 8. a) State and explain Lorentz's force equation. 5M b) Show that the force experienced by the current carrying loop placed in uniform magnetic field is zero. 9M UNIT-V 9. a) Briefly describe statically induced emf with relevant expressions 6M b) Express the differential and integral form of (i) Gauss's law for electric field (ii) Gauss's law for magnetic field (iii) Ampere's circuital law and (iv) Faraday's law. 8M OR 10. a) What is displacement current? Show that displacement current, $I_{d} = \frac{\partial D}{\partial t}$ 6M b) State the laws from which Maxwell's I, II, III and IV laws are derived and express Maxwell's equations in free space both in differential and integral form. 8M

I	Hall	Ticket Number :	
С	ode	: 4G232	
		II B.Tech. I Semester Supplementary Examinations Nov/Dec 2017 Electrical Machines-I	
		(Electrical and Electronics Engineering)	
	Mc	Time: 3 Hours Answer all five units by choosing one question from each unit (5 x 14 = 70 Marks)	5
1.		Design and draw a 2 layer progressive duplex winding with Equalizer connections for a	
		4-pole dc generator with 16 slots, each slot having 2 coil sides. Indicate the position of	
		brushes.	14M
		OR	
2.		Elucidate the principle of operation and constructional details of a machine, which generates unidirectional voltage with the neat sketch?	14M
		UNIT–II	
3.	a)	Derive the Armature ampere-turns, which cause demagnetizing effect and cross magnetizing effect for a DC machine?	8M
	b)	A 4-pole motor has a wave connected armature with 888 conductors. The brushes are	
	-,	displaced backward through 5 mechanical degrees from the geometric neutral plane. If	
		the total armature current is 90A. Calculate the cross and demagnetized ampere turns	
		per pole.	6M
4	a)	OR Illustrate the process of conversion from AC to DC in dc generators with neat diagrams?	8M
	,		
	b)	Distinguish the methods to avoid sparkings at the brushes in a DC machine?	6M
_			
5.		Sketch the internal and external characteristics of DC machine for the following applications:	
		a. suitable for consistent power supply b. Arc welding	14M
		OR	14111
6	a)	List the reasons for operating dc generators in parallel?	5M
0.	b)	Explain the process of building up of voltage in self-excited machine. Under what	
		conditions may it fail to build up the voltage?	9M
		UNIT–IV	
7.	a)	Identify the DC motor with the highest starting torque. Assess the reason with relevant equation?	8M
	b)	A 4 pole, 220V shunt motor has 540 lap wound conductors. It takes 32A from the supply	
		mains and develops output power of 5.595kw. The field winding takes 1A. The armature	
		resistance is 0.9 and the flux per pole is 30mWb. Calculate i) the speed, ii) the torque developed, iii) Shaft torque.	6M
		OR	0101
8.		Illustrate the different speed control techniques for a shunt motor?	14M
0.		UNIT-V	
٩	a)	Elaborate the test to predetermine the efficiency for a DC machine with relevant	
0.	u)	equations	8M
	b)	When running on no load, a 400V shunt motor takes 5A. Calculate the efficiency when	
	2)	the motor running on full load and taking a current of 50A. Take armature resistance as 0.5 and field resistance 200 .	6M
		OR	
10.	a)	Explain the direct test of a DC machine in detail with advantages and disadvantages?	8M
	b)	In a brake test, the dc motor took 42A from a 220V supply mains. The brake pulley of radius 30cm had an effective load of 35kg and the speed was 12rps. Find the efficiency	
		at the above load.	6M

Hall Ticket Number :					[R-14	
Code: 4GC32 II B.Tech. I Semes	ter Suppler	nentary	Examin	ations No	ov/De	ec 2017	
	Engineer	ing Mat Ion to EE					
Max. Marks: 70 Answer all five units by	·	e questio	n from ec		5 x 14 =	Time: 3 He = 70 Marks)	
1. a) Reduce the follo	wing matrix in	to its norm		nd hence f	ind its	rank	
,	$\begin{bmatrix} -1 & -1 \\ 1 & -2 & -4 \\ 3 & -2 \\ 0 & -7 \end{bmatrix}$						7M
b) Test for consiste	ncy and solve						
5x + 3y + 7z =	= 4, 3x + 26	5y + 2z =	= 9, 7 <i>x</i> +	+2y+10	<i>z</i> = 5		7M
2. a) Solve $2x - y + $	3z = 0 $x + y$	OF		- 2 by 6	201100	elimination	
method.	•		·	·			7M
^{b)} Verify Caley-Har	nilton theoren	n for the r	matrix A =	$=\begin{bmatrix} 2 & -1 \\ -1 & 2 \\ 1 & -1 \end{bmatrix}$	$\begin{vmatrix} 1 \\ -1 \\ 2 \end{vmatrix}$	and find its	;
inverse.				L	L		7M
		UNI					
 a) Find a real root correct to four de 		on $3x = c$	$\cos x + 1$ b	y Newton	-Raphs	son method	1 7M
b) Apply Runge-Ku		o find an	approxima	ate value	of v fo	or $x = 0.2$ in	
_							
steps of 0.1 if $\frac{d}{d}$	x = x + y, gi			x = 0.			7M
4. a) Find a root of	the equation	OF		aina tha	Diagoti	ion mothod	1
correct to three of			<i>J</i> = 0, u	sing the	DISECU		7M
b) Find by Taylor's				x = 0.1 a	nd <i>x</i> =	= 0.2 to five)
decimal places fi	$\operatorname{rom} \frac{dy}{dx} = x^2 y$	-1, y(0)	=1.				7M
		UNIT					,
5. a) Estimate the val				following	table b	y Newton's	;
forward and back x	20 25 354 332	30	ula: 35 260	40 231	45 204		7M
b) Use Simpson's(I	/3)rd rule and	d Simpso	n's(3/8) <i>th</i>	rule to es	stimate	$\int_{-\infty}^{6} \frac{dx}{(1+x^2)}$	
		OF				0 ()	7M

6. a) Use Lagrange's Interpolation formula to estimate f(10) from the following table:

x	5	6	9	11
f(x)	12	13	14	16

7M

7M

b) Find $\frac{dy}{dx}$ and $\frac{d^2y}{dx^2}$ at x=1.1 from the following table:

9.

x	1.0	1.1	1.2	1.3	1.4	1.5	1.6	
У	7.989	8.403	8.781	9.129	9.451	9.750	10.031	7N
			UN					

7. a) Fit a second degree parabola to the following data by the method of least squares:

x	0	1	2	3	4
у	1	1.8	1.3	2.5	6.3

b) Form the partial differential equations (by eliminating the arbitrary constants and arbitrary functions) from

$$(i)z = a x + b y + a^{2} + b^{2}$$
 and $(ii)z = f(x + a y) + g(x - a y)$ 7M

OR

8. a) Fit a curve $y = a e^{bx}$ to the following data by the method of least squares:

x	1	2	3	4
У	1.65	2.7	4.5	7.35

b) Solve $\frac{\partial u}{\partial x} = 2 \frac{\partial u}{\partial t} + u$ where $u(x,0) = 6 e^{-3x}$ by variable separable method. 7M

a) Obtain the Fourier series for the function
$$f(x) = x - x^2$$
 in the interval $[-f, f]$.
Hence show that $\frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \frac{1}{4^2} + \dots = \frac{f^2}{12}$.

b) Find the Fourier sine transform of the function $f(x) = \frac{e^{-ax}}{x}$, a > 0. 7M

OR

- 10. a) Find the half-range Cosine series for the function $f(x) = (x-1)^2$ in the interval (0,1). Hence show that $\frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots = \frac{f^2}{6}$ 7M
 - b) Show that $e^{-\binom{x^2/2}{2}}$ is a self-reciprocal with respect to Fourier Transform. 7M

	Hall Ticket Number :											
--	----------------------	--	--	--	--	--	--	--	--	--	--	--

Code: 4G231

II B.Tech. I Semester Supplementary Examinations November 2017

Switching Theory and Logic Design

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

R-14

Answer all five units by choosing one question from each unit ($5 \times 14 = 70$ Marks)

UNIT-I

- 1. a) i. Convert the hexadecimal number 68BE to binary and convert it from binary to octal
 - ii. Express the number $(26.24)_8$ in decimal.
 - iii. Implement AND Gate using NOR Gates
 - b) Obtain the
 - i. 1's and 2's complement of 11011010
 - ii. 9's and 10's complement of 12345678
 - ^{iii.} State Demorgans theorem for 3 variables

OR

- 2. a) i. Generate Hamming code for the given 11 bit message 10001110101 and rewrite the entire message with hamming code
 - ii. Draw the switching circuits for two way staircase
 - b) i. Convert the following to Decimal.
 (A) (10111111)₂ (B) (352)₈
 - ii. Write 3 properties of XOR gate
 - iii. Distinguish between weighted codes and unweighted codes

UNIT-II

- 3. a) Simplify the following using Tabular method
 F(A, B, C, D, E) = (0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 2, 31)
 - b) Reduce the expression $f = A\left(B + \overline{C}\left(\overline{AB + A\overline{C}}\right)\right)$ using Boolean theorems.

OR

- 4. a) Minimize the function $f = \Sigma m(0,2,4,6,7,8,10,12,13,15)$ using K-Map. Implement using NAND gates.
 - b) Implement the Boolean expression of EX-OR gate using minimum number of NAND gates.

5. a) Implement the function $F(A,B,C,D) = \frac{UNIT-III}{AB + BD + BCD} | 8 \times 1 \text{ multiplexer}$

b) Design a 4-bit Binary to Gray code converter.

OR

- 6. a) Design a full adder using Half adder. Give internal logic function and Truth Table
 - b) Implement the following unction using PLA

 $\begin{array}{lll} A(x\,,\,y\,,\,z) = & m(1,\,2,\,4,\,6) \\ B((x\,,\,y\,,\,z) = & m(0,\,1,\,6,\,7) \\ C((x\,,\,y\,,\,z) = & m(2,\,6) \end{array}$

UNIT-IV

- 7. a) Convert JK-flip flop to D-flip flop.
 - b) Design a mod-6 synchronous counter using JK-flip flop.

OR

- 8. a) Design a mod-8 synchronous counter using D flip-flops.
 - b) Draw the excitation tables of SR, T and D-flip flop.

UNIT-V

- 9. a) List the capabilities and limitations of finite state machines.
 - b) Draw and explain ASM chart of a mod-6 counter.

OR

- 10. a) Draw the state diagram and state table for a sequence detector which can detect a sequence 101.
 - b) Minimize the following state table using partition method.

Next state, Output					
x = 0	x = 1				
b, 0	d, 1				
g, 0	a, 0				
d, 0	b, 1				
g, 0	a, 0				
d, 0	a, 1				
e, 1	f, 1				
d, 1	d, 1				
	x = 0 b, 0 g, 0 d, 0 g, 0 d, 0				
