Hall Ticket Number :						D 14
						R-14

Code: 4G235

II B.Tech. I Semester Supplementary Examinations Nov/Dec 2017

Electrical Circuit Theory

(Electronics and Communication Engineering)


Max. Marks: 70

Time: 3 Hours


Answer all five units by choosing one question from each unit (5 x 14 = 70 Marks)



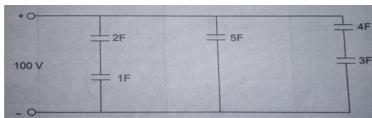1 a) Find the total equivalent capacitance, total energy stored if the applied voltage is 100V for the circuit as shown in Fig.



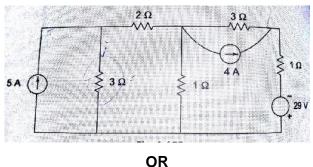
b) Write and solve the equation for mesh current in network.




7M

7M

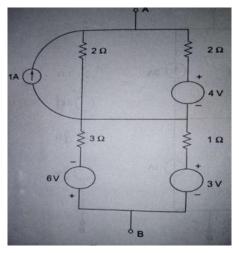2. a) Using source transformation, reduce the network between A and B into an equivalent voltage source.



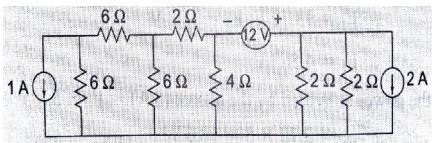b) Find the power supplied by 12V source as shown in fig. below




7M


8M



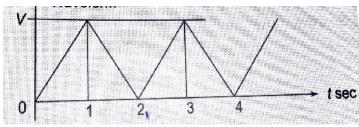
3. a) Find the form factor for the following waveform.



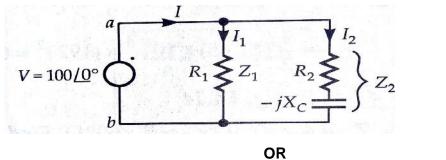
b) In below fig R₁=3 ohms, R₂=10 ohms, and $-jX_c=-j8$ ohms. Find I₁, I₂ and I. also obtain Z_{eq} across a-b.



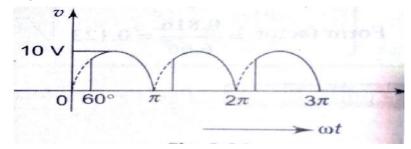4. a) The full wave rectified sine wave shown in below fig. has a delay angle of 60° . Calculate V_{avg} and V_{rms}.



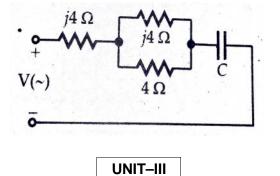
b) What should be the value of C such that the input power factor is unity for any frequency of the source?



6M

8M

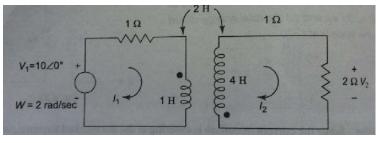- 5. a) Derive the expression for coefficient coupling between pair of magnetically coupled coils. 6M
 - b) Solve for the currents I_1 and I_2 in the circuit shown in Fig. Also, find the ratio of V_2/V_1 .



8M

7M


7M

7M

7M

6M

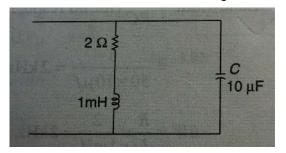6. a) In the parallel resonant circuit, determine the resonance frequency, dynamic resistance and bandwidth for the circuit shown in Fig. 3.



b) In a series RLC circuit R=1K , L-120mH, and c=12 $\mu\mu$ F. If a voltage of 200V is applied across the combination, determine

i) Resonant frequency

ii)Q factor

- iii) Half Power Frequencies
- iv) Band width and
- v) The voltage across the inductance and the capacitance

UNIT–IV


- A three phase balanced system supplies 110V to a delta connected load whose phase impedances are equal to (3.54+j3.54) ohm. Determine the line currents and draw the phasor diagram.
 - b) A star connected alternator supplies a delta connected load. The impedance of each branch is (6+j8) ohm. The line voltage is400V. Obtain the current in phase of the load. Also find the current in each phase of the alternator. What is the power drawn by the load and its power factor? Determine the reactive power of the load.

OR


- 8. a) The phase impedance of a delta connected load is (15+j20) ohms. What is the line current if the applied line voltage is 220V? Obtain the amount of power consumed per phase. What is the phasor sum of the three line currents?
 - b) A star-connected alternator has 231V/Ph. It supplies a set of lighting loads at phase R, having phase impedance of 40∠0° ohms, a capacitive load of 10∠-60° ohm at phase Y and an inductive load of 5∠45° ohm at phase B. The loads are connected in delta. Obtain the phase currents, line currents and line voltages.



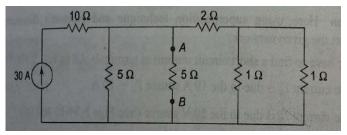
- 9. a) Explain the steps to apply Thevenin's theorem and draw the Thevenin's equivalent circuit.
 - b) Determine the current flowing through the 5ohms resistor in the circuit shown in Fig. by using Norton's theorem.



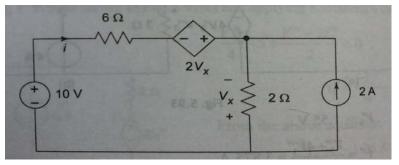10. a) Find the current I in the circuit shown in Fig. using superposition theorem.



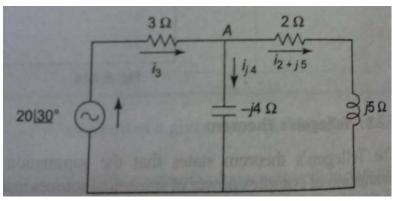b) Verify Tellegen's theorem for the network shown in Fig



8M

Hall Ticket Number :						R-14	
Code: 4GC32 II B.Tech. I Semeste	er Suppler	nentary	Examin	ations N	ov/De	ec 2017	
	Engineer	ing Mat Ion to EE					
Max. Marks: 70 Answer all five units by c	•	e questio	n from ec		5 x 14 :	Time: 3 H = 70 Marks	
1. a) Reduce the follow	ng matrix int	UNI to its norm		nd hence t	find its	rank	
$A = \begin{bmatrix} 2 & 3 \\ 1 & -1 \\ 3 & 1 \\ 6 & 3 \end{bmatrix}$							7M
b) Test for consistent	cy and solve						
5x + 3y + 7z = 4	4, 3x + 26	5y + 2z =	= 9, 7x -	+2y+10	<i>z</i> = 5		7M
2. a) Solve $2x - y + 3$	z = 0 $x + y$	OF		-) by (201100	elimination	`
method.			·	-			7M
b) Verify Caley-Ham	lton theoren	n for the	matrix A	$=\begin{bmatrix} 2 & -1 \\ -1 & 2 \\ 1 & -1 \end{bmatrix}$	$\begin{vmatrix} 1 \\ -1 \\ 2 \end{vmatrix}$	and find its	3
inverse.				L			7M
	_	UNI					
a) Find a real root o correct to four dec		on $3x = c$	$\cos x + 1$ k	by Newton	-Raph	son method	d 7M
b) Apply Runge-Kutt		o find an	approxim	ate value	of v f	or $x = 0.2$ ir	
steps of 0.1 if $\frac{dy}{dx}$	-x+y, gr			she $x = 0$.			7M
4. a) Find a root of th		OF		uning the	Diagot	ion mothor	4
correct to three de			- <u>J</u> =0, t	ising the	DISECI		л 7М
b) Find by Taylor's s				x = 0.1 a	and x =	= 0.2 to five	Э
decimal places fro	$m\frac{dy}{dx} = x^2 y$	-1, y(0)	=1.				7M
	cust.	UNIT					,
5. a) Estimate the value				following	table b	by Newton's	3
forward and backv $\begin{array}{c} x\\ f(x) \end{array}$	ard interpol 20 25 354 332	30	iula: 35 260	40 231	45 204	_	7M
b) Use Simpson's (1/3	s)rd rule and	d Simpso	n's(3/8) <i>th</i>	i rule to es	stimate	$= \int_{a}^{6} \frac{dx}{(1+x^2)}$	
		OF				0()	7M

6. a) Use Lagrange's Interpolation formula to estimate f(10) from the following table:

x	5	6	9	11
f(x)	12	13	14	16

7M

b) Find $\frac{dy}{dx}$ and $\frac{d^2y}{dx^2}$ at x=1.1 from the following table:

9.

x	1.0	1.1	1.2	1.3	1.4	1.5	1.6	
У	7.989	8.403	8.781	9.129	9.451	9.750	10.031	7N
			UN	IIT–IV				

7. a) Fit a second degree parabola to the following data by the method of least squares:

x	0	1	2	3	4
у	1	1.8	1.3	2.5	6.3

b) Form the partial differential equations (by eliminating the arbitrary constants and arbitrary functions) from

$$(i)z = a x + b y + a^{2} + b^{2}$$
 and $(ii)z = f(x + a y) + g(x - a y)$ 7M

OR

8. a) Fit a curve $y = a e^{bx}$ to the following data by the method of least squares:

x	1	2	3	4
У	1.65	2.7	4.5	7.35


b) Solve $\frac{\partial u}{\partial x} = 2 \frac{\partial u}{\partial t} + u$ where $u(x,0) = 6 e^{-3x}$ by variable separable method. 7M

a) Obtain the Fourier series for the function
$$f(x) = x - x^2$$
 in the interval $[-f, f]$.
Hence show that $\frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \frac{1}{4^2} + \dots = \frac{f^2}{12}$.

b) Find the Fourier sine transform of the function $f(x) = \frac{e^{-ax}}{x}$, a > 0. 7M

OR

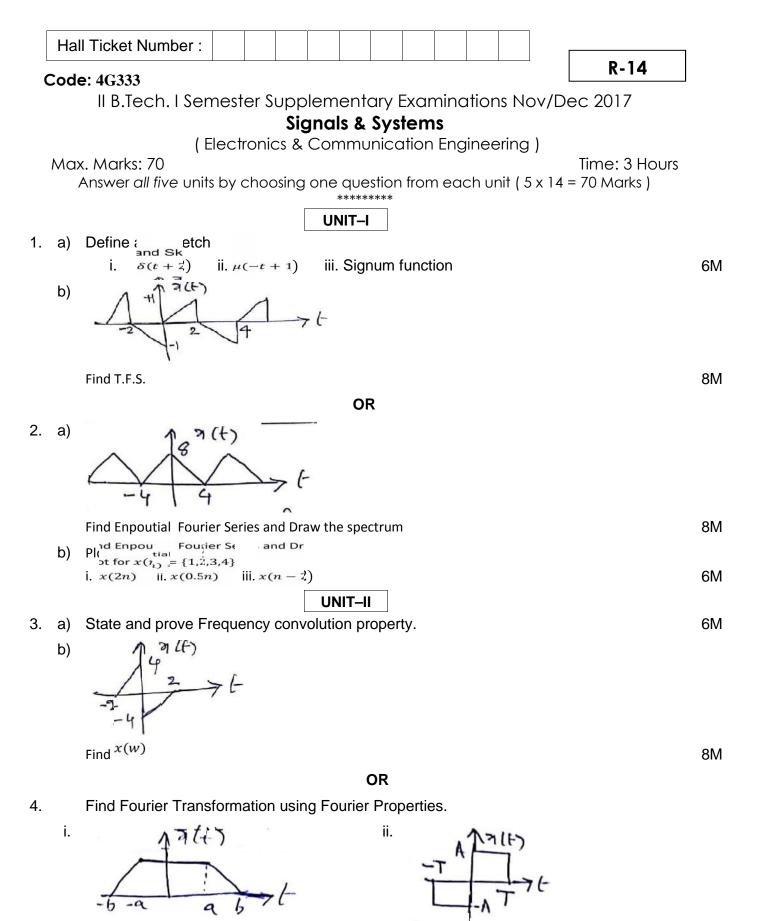- 10. a) Find the half-range Cosine series for the function $f(x) = (x-1)^2$ in the interval (0,1). Hence show that $\frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots = \frac{f^2}{6}$ 7M
 - b) Show that $e^{-\binom{x^2/2}{2}}$ is a self-reciprocal with respect to Fourier Transform. 7M



6M

6M


5. a) T_{i} L inearity, Ti_{i} ance $UNIT_{i}$ and cal ility for $i. y(t) = [x(t)]^2$ ii. $y(t) = \log_{10}[x(t)]$ iii. $y(t) = \sin_{10} at$ 6M b) Explain Paley-Weiner Criterion. 8M

OR

- - b) Derive the condition for Distortion less Transmission and draw the magnitude & phase characteristics.
 8M

UNIT–IV

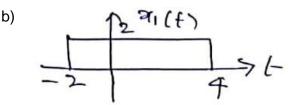7. a) Write Differences between auto and cross correlation and state any four properties of auto correlation.



Find autocorrelation.

OR

- 8. a) Find the energy spectral density of the signal x(t) = 10) so find its total energy. 6M
 - b) Define sampling theorem $\lim_{\text{for time}} \lim_{ited signal}$ and find the Nyquist rate for i. rect 300t ii. $10 \sin 10\pi t \cos 300 \frac{\pi t}{\pi t}$

UNIT-V

9. a) $\begin{array}{c} \stackrel{\text{i. rect:}}{F(S) = \frac{10}{s(s+10)}, \text{ find unit ramp response of the system.}}{F(S) = \frac{10}{s(1+\frac{1}{1-5}), \frac{1}{1-\frac{1}{2}}, \frac{1}{2}}, \frac{1}{1-\frac{1}{2}}, \frac{1}$

OR

- 10. a) State and prove initial and final value theorem using L.T.
 - b) state p_{-c} we initial p_{-c} value the [rem using L.T10)] $t_{-x}(n) = 2^n \frac{u(-n-1)}{u(-n-1)}$ $u_{-x}(n) = u(n) - u(n-1)$ Find x(Z) and show Region of Convergence.
