

Hall Ticket Number :

R-19

Code: 19A433T

II B.Tech. I Semester Regular Examinations March 2021

**Digital Design**

( Electronics and Communication Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

	Marks	CO	Blooms Level
<b>UNIT-I</b>			
1. a) Explain about even and odd parity check with an example, what is the drawback	7M	1	L2
b) Express the following numbers in decimal: $(10110.0101)_2$ , $(16.5)_{16}$ , $(26.24)_8$ .	7M	1	L2
<b>OR</b>			
2. a) Perform subtraction with the following unsigned decimal numbers by taking 10's complement of the subtrahend. Verify the result. i. $5250 - 1321$ ii. $1753 - 8640$ iii. $20 - 100$ iv. $1200 - 250$	7M	2	L5
b) Convert the following to require form i) $(163.789)_{10} = ( )_8$ ii) $(101101110001.00101)_2 = ( )_8$ iii) $(292)_{16} = ( )_2$ iv) What is meant by self-complementing codes.	7M	2	L5
<b>UNIT-II</b>			
3. a) Obtain the simplified expression in sum of products for the following Boolean function. i) $F(A,B,C,D) = (2,3,12,13,14,15)$ . ii) $BDE + BC D + CDE + A B CE + A B C + B C D E$	7M	1	L2
b) Implement the function $f(a,b,c) = (0,1,3,4)$ using NAND-NAND two level gate structure.	7M	2	L5
<b>OR</b>			
4. a) Obtain the minimal sum of products expression for the following function and implement the same using only NAND gates $f(A, B, C, D) = \sum (1,4,7,8,9,11) + \sum d(0,3,5)$	7M	2	L5
b) Obtain minimal POS expression for the given Boolean function $f(A,B,C,D) = \sum (1, 2, 3, 4, 8, 9, 12)$ And draw the circuits with two Level NOR-NOR form and AND - OR form.	7M		
<b>UNIT-III</b>			
5. a) Realize a full subtractor using decoder.	7M	4	L2
b) Draw the logic diagram of 2:4 Decoder with an ENABLE input using: i) NAND gates ii) AND gates. Show that the realization using NAND gates is more convenient to distinguish the selected output with a value of 0.	7M	2	L5
<b>OR</b>			
6. a) Tabulate the truth table for 8*4 ROM to input the following functions: $A = (1,2,4,6)$ $B = (0,1,6,7)$ $c = (2,6)$ $D = (1,2,3,5,7)$	7M	1	L2
b) Design a 4 bit BCD adder using Full adder circuits	7M	3	L6

<b>UNIT-IV</b>
----------------

7. a) Design and explain Johnson counter. 6M 3 L6  
 b) Design mod-10 synchronous counter using D-FlipFlops. 8M 1 L2

OR

8. a) Write the differences between asynchronous and synchronous sequential circuits. 7M 2 L5  
 b) Give the implementation procedure for a SR Latch using NOR gates. 7M 2 L5

<b>UNIT-V</b>
---------------

9. a) Discuss Moore Machine models of sequential circuits. 7M 2 L5  
 b) What are the capabilities and limitations of finite state machines? Explain. 7M 4 L2

OR

10. a) Reduce the number of states in the following state table and tabulate the reduced state table.

PS	NS, O/P	
	X=0	X=1
a	f, 0	b, 0
b	d, 0	c, 0
c	f, 0	e, 0
d	g, 1	a, 0
e	d, 0	c, 0
f	f, 1	b, 1
g	g, 0	h, 1
h	g, 1	a, 0

7M 3 L6

- b) Obtain the state table and state diagram for a sequence detector to recognize the occurrence of sequence bits 110 & 001. 7M 2 L5

\*\*\*\*

**Code: 19A237T**

II B.Tech. I Semester Regular Examinations March 2021

**Electrical Circuits and Technology**

( Electronics and Communication Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )


\*\*\*\*\*

**UNIT-I**

1. a) Derive the expression for star and delta transformation
- b) Find current (I) flowing through the 4 ohm resistor using nodal analysis

Marks    CO    Blooms Level


7M    CO1    L1

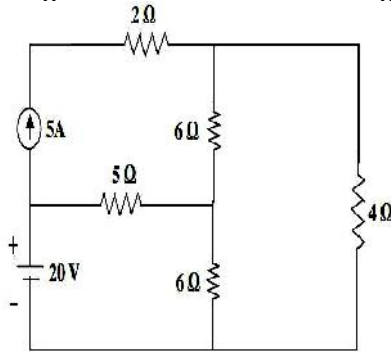

7M    CO1    L2

**OR**

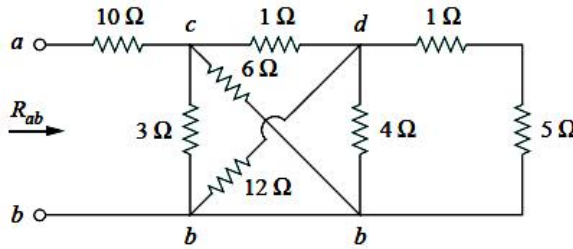2. a) Calculate the equivalent resistance  $R_{ab}$  in the below circuit




7M    CO1    L1

- b) Explain the step response of an RL circuit using differential approach for DC excitation.

7M    CO1    L3

**UNIT-II**

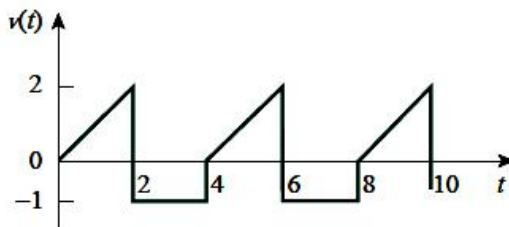3. a) Determine the Average value & RMS value, peak factor and form factor of the below waveform.



7M    CO2    L2

- b) Explain the importance of sinusoidal waveforms and list out the Advantages of AC supply.

7M    CO2    L3

**OR**


4. a) Define the following terms:
  - i) Resonant frequency ii) Band Width iii) Quality factor
- b) Explain the parallel resonance of RLC circuit with suitable wave form and equations.

6M    CO2    L3

8M    CO2    L2

<b>UNIT-III</b>
-----------------

- |    |  |    |     |    |
|----|--|----|-----|----|
| 5. | a) Derive the condition of reciprocity and symmetry for y-parameters | 7M | CO3 | L1 |
|    | b) Find the impedance-parameter equivalent of the circuit.           |    |     |    |

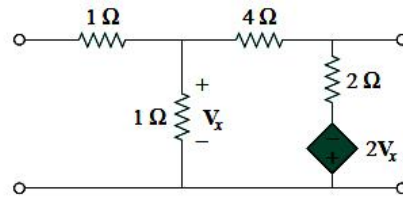

		7M	CO3	L2
--	--	----	-----	----

**OR**

- |    |  |    |     |    |
|----|--|----|-----|----|
| 6. | a) Find the relationship between impedance parameters and h-parameters.                              | 7M | CO3 | L2 |
|    | b) The Z parameters are $Z_{11}=4$ , $Z_{12}=6$ , $Z_{21}=3$ , $Z_{22}=8$ , find A,B,C,D parameters. | 7M | CO3 | L3 |

<b>UNIT-IV</b>
----------------

- |    |  |     |     |    |
|----|--|-----|-----|----|
| 7. | a) Explain the constructional features and operation of a DC generator with diagram. | 10M | CO4 | L3 |
|    | b) Draw magnetization characteristics and application of DC generator.               | 4M  | CO4 | L1 |

**OR**

- |    |   |    |     |    |
|----|---|----|-----|----|
| 8. | a) Derive an expression for torque developed in the armature of DC motor. | 7M | CO4 | L3 |
|    | b) Derive the EMF equation of DC generator                                | 7M | CO4 | L2 |

<b>UNIT-V</b>
---------------

- |    |   |    |     |    |
|----|---|----|-----|----|
| 9. | a) Explain how efficiency of a static machine can be predetermined by suggesting suitable method. | 7M | CO5 | L3 |
|    | b) Derive the EMF equation of a transformer   | 7M | CO5 | L2 |
- OR**
- |     |  |    |     |    |
|-----|--|----|-----|----|
| 10. | a) Discuss about the slip torque characteristics of a three phase induction motor. | 7M | CO5 | L3 |
|     | b) Explain the brake test on three phase induction motor.                          | 7M | CO5 | L1 |

\*\*\*\*\*

Hall Ticket Number :

--	--	--	--	--	--	--	--	--	--

R-19

Code: 19A431T

II B.Tech. I Semester Regular Examinations March 2021

**Electronic Circuits**

( Electronics and Communication Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

	Marks	CO	Blooms Level
<b>UNIT-I</b>			
1. a) List out the different coupling schemes in amplifiers and explain them.	10M	CO1	L1
b) State and prove Miller's and dual of Miller's theorem.	4M	CO1	L2
<b>OR</b>			
2. a) Draw and explain small signal equivalent of BJT common emitter circuit.	7M	CO1	L3
b) Give analysis about CB and CC configuration in terms of h- parameters using simplified model.	7M	CO1	L1
<b>UNIT-II</b>			
3. a) Draw the circuit diagram and equivalent circuit for current shunt feedback amplifier and derive the expression for total voltage gain	7M	CO1	L3
b) What are the different characteristics of negative feedback amplifiers? Discuss in brief	7M	CO2	L1
<b>OR</b>			
4. a) Draw the block diagrams of the four possible feedback topologies and explain.	7M	CO2	L3
b) Prove that the bandwidth of the amplifier increases with negative feedback.	7M	CO2	L5
<b>UNIT-III</b>			
5. a) Explain working of Hartley oscillator. Derive an Expression for frequency of oscillation and condition for oscillation	7M	CO2	L1
b) Classify the different oscillators and draw their diagrams.	7M	CO2	L6
<b>OR</b>			
6. a) Draw circuit diagram of RC phase shift oscillator and explain its operation by deriving expression for frequency of oscillation.	10M	CO2	L3
b) Describe operation of crystal oscillators.	4M	CO3	L2
<b>UNIT-IV</b>			
7. a) Explain the working of Series fed, directly coupled Class-A power amplifier with the help of a neat circuit diagram.	7M	CO3	L1
b) Give the expression for dc power input, ac power output and its efficiency of directly coupled Class-A amplifier?	7M	CO3	L1
<b>OR</b>			
8. a) Explain the push-pull Class-B power amplifier with neat sketches of load line.	10M	CO3	L1
b) Mention some of the important applications of Class-B amplifier.	4M	CO4	L3
<b>UNIT-V</b>			
9. a) Explain the operation of high pass RC circuits for a square wave input with the circuit diagram and waveforms.	7M	CO4	L1
b) Derive the expression for high pass RC circuit with Ramp input.	7M	CO4	L2
<b>OR</b>			
10. a) Design any three different positive and negative clipper circuits with and without biasing and also draw the corresponding input and output waveforms and transfer characteristics	7M	CO4	L3
b) State and prove Clamping circuit theorem.	7M	CO4	L1

\*\*\*\*

**Code: 19AC31T**

II B.Tech. I Semester Regular Examinations March 2021  
**Partial Differential Equations and Complex Variables**  
 ( Common to CE, EEE, ME & ECE )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

Marks    CO    Blooms Level

**UNIT-I**

- |   |    |     |    |
|---|----|-----|----|
| 1. a) Find the Laplace Transform of $f(t) = \begin{cases} \cos t, & 0 < t < f \\ \sin t, & t > f \end{cases}$ | 7M | CO1 | L1 |
| b) Find $L \left( \frac{\cos 2t - \cos 3t}{t} \right)$  | 7M | CO1 | L1 |

**OR**

- |   |    |     |    |
|---|----|-----|----|
| 2. a) Find the Laplace transform of $e^{4t} (\sin 2t \cos t)$   | 7M | CO1 | L1 |
| b) Find the Laplace transform of $f(t) = \begin{cases} 1, & 0 \leq t < 1 \\ -1, & 1 \leq t < 2 \end{cases}$ having period 2 | 7M | CO1 | L1 |

**UNIT-II**

- |  |    |     |    |
|--|----|-----|----|
| 3. a) Find the inverse Laplace Transform of $\frac{1}{(s^2 + 1)s}$                         | 7M | CO2 | L1 |
| b) Apply Convolution theorem to evaluate $L^{-1} \left\{ \frac{s}{(s^2 + a^2)^2} \right\}$ | 7M | CO2 | L3 |

**OR**

- |   |     |     |    |
|---|-----|-----|----|
| 4. Solve $\frac{d^2 y}{dt^2} + 2 \frac{dy}{dt} + 2y = 5 \sin t$ , if $y(0) = y'(0) = 0$ | 14M | CO2 | L3 |
|---|-----|-----|----|

**UNIT-III**

- |  |     |     |    |
|--|-----|-----|----|
| 5. Expand $f(x) = x - x^2$ as Fourier series in the interval $(-f, f)$ and hence obtain $\frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \frac{1}{4^2} + \dots = \frac{f^2}{12}$ | 14M | CO3 | L3 |
| <b>OR</b>  |     |     |    |
| 6. a) Find a Fourier series to represent $f(x) = x \sin x$ , $-f < x < f$ and hence deduce that $\frac{1}{1.3} - \frac{1}{3.5} + \frac{1}{5.7} - \dots = \frac{1}{4}(f - 2)$     | 7M  | CO3 | L1 |
| b) Express $f(x) = x^2$ as half-range sine series in $0 < x < 4$   | 7M  | CO3 | L2 |

**UNIT-IV**

- |   |     |     |    |
|---|-----|-----|----|
| 7. If a string of length $\ell$ is initially at rest in the equilibrium position and each of its points is given, the velocity $V_0 \sin^3 \frac{fx}{\ell}$ find the displacement $y(x, t)$ .   | 14M | CO4 | L2 |
| <b>OR</b>   |     |     |    |
| 8. An insulated rod of length $\ell$ has its ends A and B maintained at $0^\circ\text{C}$ and $100^\circ\text{C}$ respectively until steady state condition prevails. If B is suddenly reduced to $0^\circ\text{C}$ and maintained at $0^\circ\text{C}$ , Find the temperature at a distance $x$ from A at time $t$ . | 14M | CO4 | L3 |

**UNIT-V**

- |  |     |     |    |
|--|-----|-----|----|
| 9. Show that the function $f(z) = \begin{cases} \frac{x^3(1+i) - y^3(1-i)}{x^2 + y^2}, & \text{if } z \neq 0 \\ 0, & \text{if } z = 0 \end{cases}$ is not analytic at origin, even though C-R equations are satisfied at origin. | 14M | CO5 | L2 |
| <b>OR</b>  |     |     |    |
| 10. a) Show that the function $v(x, y) = \sin x \cosh y + 2 \cos x \sinh y + x^2 - y^2 + 4xy$ satisfies Laplace equation and find the corresponding analytic function $u + iv$   | 7M  | CO5 | L1 |
| b) Verify Cauchy's theorem for the function $f(z) = 3z^2 + iz - 4$ taken over the boundary of the square with vertices $1 \pm i$ and $-1 \pm i$  | 7M  | CO5 | L4 |

\*\*\*\*







<b>UNIT-III</b>
-----------------

- |  |    |   |    |
|--|----|---|----|
| 5. a) What are the characteristics of ideal LPF and HPF  | 6M | 1 | L1 |
| b) The response of a continuous time LTI system is $2e^{-3t}$ when the input $x(t)$ is $u(t)$ find the Transfer function | 8M | 3 | L4 |

**OR**

- |  |    |   |    |
|--|----|---|----|
| 6. a) What is the different classification of Sampling? Explain each with neat sketch. | 8M | 1 | L1 |
| b) What is mean by aliasing? How would you eliminate it? Explain.                      | 1  |   | L2 |

<b>UNIT-IV</b>
----------------

- |  |    |   |    |
|--|----|---|----|
| 7. a) State the condition for Stability of any system and derive an expression for same. | 6M | 2 | L3 |
| b) Find the convolution of the following signals   |    |   |    |
| i) $x_1(t) = e^{-3t}u(t)$ and $x_2(t) = u(t+3)$  |    |   |    |
| ii) $x_1(t) = e^{-at}u(t)$ $x_2(t) = e^{-bt}u(t)$  | 8M | 3 | L4 |

**OR**

- |   |    |   |    |
|---|----|---|----|
| 8. a) State and prove the relation between auto correlation function and energy / power spectral density function | 7M | 2 | L2 |
| b) Write the properties of cross Correlation for periodic signal  | 7M | 4 | L1 |

<b>UNIT-V</b>
---------------

- |   |    |   |    |
|---|----|---|----|
| 9. a) Explain the Linearity and time shifting properties of Laplace transform.            | 7M | 5 | L2 |
| b) Find the Laplace transform of $t u(t)$ . List properties of ROC for Laplace transforms | 7M | 5 | L4 |

**OR**

- |   |    |   |    |
|---|----|---|----|
| 10. a) Find the Z-transform of the given signal $x(n)$ and find ROC: $X(z) = [\sin(\omega_0 n)] u(n)$ | 7M | 5 | L3 |
| b) Find the inverse Z- transform of $X(z) = \frac{1+3z^{-1}}{1+3z^{-1}+2z^{-2}}$                      | 7M | 4 | L4 |

\*\*\*\*\*