Hall	Tic	ket Number :												
Code: 1G431														
COU	•••	II B.Tech. I Semester Supplementary Examinations May 2019												
		Digital Logic Design and Computer Organization												
Max	x. M	( Information Technology ) 1arks: 70 Time: 3	Hours											
		Answer any <b>five</b> questions												
		All Questions carry equal marks ( <b>14 Marks</b> each)												
1.	a)	) List out differences between Multiprocessors and Multi computers.												
	b)	) I. Convert to Binary:												
		i) (12A4) <sub>16</sub> ii) (1724) <sub>8</sub> iii) (101) <sub>10</sub> II. Convert to Hexadecimal:												
		iv) $(0101011)_2$ (v) $(612)_8$	8M											
2.	<b>a</b> )	Implement the following Boolean function F using no more than two NOF	<b>.</b>											
۷.	a)	gates and draw the circuit.	<b>\</b> -											
		F (A,B,C,D) = P(0, 1, 2, 9, 11) + d (8, 10, 14, 15)	7M											
	b)	Obtain the complement of the following Boolean expressions:												
		i. A'B + A'BC' + A'BCD + A'BC'D'E ii. ABEF + ABE'F' + A'B'EF.	7M											
3.	a)	<ul> <li>Design a 4-bit ring counter using T-flip flops and draw the circuit diagram and timing diagrams.</li> </ul>												
	b)	) With logic diagram explain how a Demultiplexer can be obtained from a Decoder.												
4	a)	a) Explain the hardware algorithm to perform multiplication of two binary numbers												
ч.	u)	with help of a flow chart. Multiply 10111 with 10011 with the above procedu												
		given. Show all the registers content for each step.	7M											
	b)	b) Explain Arithmetic subtraction with an example.												
5.	a)	Explain various phases of Instruction Cycle.	7M											
	b)	b) Explain different addressing modes with suitable examples.												
6.	a)	a) With an example explain microprogrammed control unit.												
	b)	What are the two different ways to construct a common bus structure a												
		explain each with a neat sketch?	7M											
7.	,	Explain about performance considerations in memory system.												
	b)	Write the concept of virtual memory and explain the page replacement algorithms in virtual memory.	ent 7M											
8.	a)	(i) What is Direct Memory Access? Explain the working of DMA.												
		(ii) What are the different kinds of DMA transfers? Explain.	7M											
	b)	What are the different modes of data transfer? Explain each mode in detail.	7M											

Hall Ticket Number :														Г		
Code: 1G334								R-11 / R-13								
II B.Tech. I Semester Supplementary Examinations May 2019																
Electronic Devices and Circuits																
( Common to CSE & IT ) Max. Marks: 70 Time:										Time: (	3 Hours					
Answer any <b>five</b> questions																
	All Questions carry equal marks ( <b>14 Marks</b> each)															
1.	. a) Distinguish between Zener Break down and Avalanche Break down											own.				
	b)	Draw the Zener diode V-I characteristics. Explain how Zener diode provides a											а			
		constant output voltage.														
2.	a)	Draw the circuit diagram of Half-Wave rectifier and explain its operation														
	b)	List out the differences between Half wave and Full wave rectifier														
3.	a)	) Derive the relationship between $a_{c}$ and $d_{c}$ .														
	b)	Construct Common Emitter configuration and derive Output characteristics														
4.	a)	a) Write short notes on														
		i) Thermal resistance														
	ь)	<ul><li>ii) Heat sink.</li><li>What are the advantages of self-bias over fixed bias?</li></ul>														
	b)	what are the	auva	ntage	35 01	sen-	Jias (	overi	ixea	DIAS	ſ					
5.	a)	With neat s						•		•	ain	the	d	Irain	& trans	fer
	b)	Establish a re				-			-		ters.	u. r	⊣ar	nd a <sub>n</sub>	n.	
	,								- I		,	<b>P</b> ., . ¢				
6.	a)	Define an am	plifier	? Lis	t vari	ous f	ypes	of A	mplif	iers?						
	b)	Draw the sma	ll sig	nal h	-para	mete	er mo	del fo	or CE	, CB	con	igura	atio	ons.		
7.	<ol> <li>a) Explain about voltage series and current series feedback.</li> </ol>															
	b)	Draw and exp	lain v	/oltag	ge se	ries f	eedb	ack.								
8.	a)	With a neat c	ircuit	diag	ram e	expla	in the	e wor	king	of R	C ph	ase s	shi	ft oso	cillator	
	b)	<ul> <li>Distinguish between Hartley and colpitts oscillator</li> </ul>														
	***															

Hall Ticket Number :											
----------------------	--	--	--	--	--	--	--	--	--	--	--

## Code: 1G133

R-11 / R-13

II B.Tech. I Semester Supplementary Examinations May 2019

Mathematical Foundations of Computer Science


Max. Marks: 70

(Common to CSE & IT)

Time: 3 Hours

## Answer any **five** questions All Questions carry equal marks (**14 Marks** each)

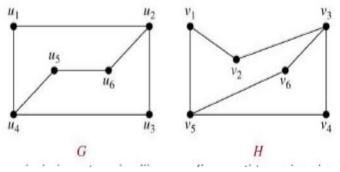- 1. a) List out the different types of connectives and explain with truth tables.
  - b) Construct the truth table for the following statement formula:
     (P Q)v(~P R)v(Q R) (~PvQ)
- 2. a) Show that **R S** can be derived from the premises **P** (**Q S**), ¬**RVP**, **Q** 
  - b) State and explain automatic theorem proving.
- 3. a) Explain properties of binary relations in a set with examples.
  - b) Explain representation of relation.
- a) On the set Q of all relational numbers, the operation \* is defined by a\*b =a+b-ab. Show that, under this operation, Q forms a commutative monoid.
  - b) Prove that the intersection of two submonoids of a monoid is a monoid.
- 5. a) Define the following with examples:
  - i) Sum rule
  - ii) Product rule
  - b) State and explain pigeon hole principle with an example.
- 6. Solve the recurrence relation  $a_n+2a_{n-1}-3a_{n-2}=4n^2-5$  for n 2, given that  $a_0=0$  and  $a_1=1$ .
- 7. a) Define a Graph and Explain the different types of representing a Graph.
  - b) Define the following with examples:
    - i) Indegree
    - ii) Out degree
    - iii) Isolated verex
    - iv) Null graph
- 8. a) Find whether the following graphs are isomorphic or not.



b) Prove that if G is a connected plane graph then |V| - |E| + |R| = 2