

**Code: 4G331**

II B.Tech. I Semester Supplementary Examinations May 2019

**Electronic Circuits**

( Electronics and Communication Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

1. a) Draw the small signal hybrid equivalent model of a transistor. Derive the expressions for  $A_i$ ,  $Z_i$ ,  $A_v$  and  $Y_o$ . 8M
- b) A CE amplifier is drawn by a voltage source of internal resistance  $R_s = 800$  and the load impedance is a resistance  $R_L = 1000$  . The h-parameters are  $h_{fe} = 50$ ,  $h_{ie} = 1 \text{ k}$  ,  $h_{oe} = 25 \mu\text{A/V}$  and  $h_{re} = 2 \times 10^{-4}$ . Calculate  $A_i$ ,  $A_v$ ,  $Z_i$  and  $Z_o$  using exact analysis. 6M

**OR**

2. Draw the circuit diagram of two stage RC coupled transistors amplifiers. Explain the operation and calculate the mid frequency range and low frequency range. 14M

**UNIT-II**

3. Determine high frequency parameters of Hybrid – model in terms of low frequency parameters. 14M

**OR**

4. a) Define Gain Bandwidth product and derive the relation between  $f_T$  and  $f$  . 7M
- b) Derive the expression for CE Short circuit current gain with the help of necessary circuit diagrams and approximations. 7M

**UNIT-III**

5. a) Derive the expression for feedback gain, input resistance and output resistance for voltage series feedback amplifier. 8M
- b) A voltage series negative feedback amplifier has a voltage gain without feedback of  $A=50$ , input resistance  $R_i= 2\text{K}$  , output resistance  $R_o= 15\text{K}$  and feedback ratio of 0.01. Calculate the voltage gain, input resistance and output resistance of the amplifier with feedback? 6M

**OR**

6. a) Prove that negative feedback increases the bandwidth and decreases the distortion. 7M
- b) An amplifier has a gain of 400,  $f_1=50\text{Hz}$ ,  $f_2=200\text{KHz}$  and a distortion of 10% without feedback. Determine the amplifier voltage gain  $f_{1f}$ ,  $f_{2f}$  and  $D_f$  when a negative feedback is applied with feedback ratio of 0.01. 7M

**UNIT-IV**

7. a) With a neat circuit diagram, explain the generalized analysis of LC oscillator. 8M
- b) Colpitt's oscillator is designed with  $C_2=100 \text{ pF}$ ,  $C_1= 7500\text{pF}$  and a variable inductance. Determine the range of inductance values, if the frequency of oscillation is varied between 950 KHz and 2050 KHz. 6M

**OR**

8. a) Classify various types of oscillators. Explain in brief. 6M
- b) Show that the gain of Wein-bridge oscillator using BJT amplifier is at least 3 for oscillations to occur. 8M

**UNIT-V**

9. a) Show the conversion efficiency of transformer coupled class A amplifier is 50%. 8M
- b) Explain the operation of Class B push pull amplifier. 6M

**OR**

10. Describe the operation of a single tuned capacitive coupled amplifier and derive the expression for bandwidth. 14M

\*\*\*

Hall Ticket Number :										
----------------------	--	--	--	--	--	--	--	--	--	--

**R-14**

**Code: 4G235**

II B.Tech. I Semester Supplementary Examinations May 2019

**Electrical Circuit Theory**

( Electronics and Communication Engineering )

Max. Marks: 70


Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

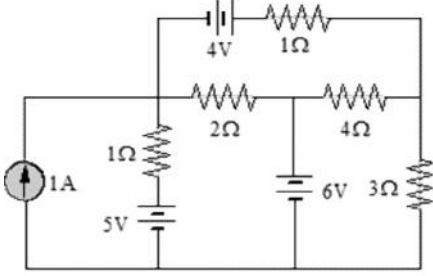1. Determine the current through 3 ohms resistor using node voltage analysis



**OR**

2. Explain about Star &Delta transformations with equations.

**UNIT-II**

3. a) Explain the advantages of AC supply  
 b) A series circuit consisting of a resistor of 10 ohms and an inductance of 100mH is connected across a 200V, 50Hz, single phase ac supply. Determine the current drawn, real power and reactive power

**OR**

4. a) Define Cycle, Time Period, Frequency, Peak to Peak value & Amplitude with wave forms.  
 b) A voltage wave is represented by  $v=200\sin314t$ . Find i)Maximum value ii)RMS value iii) Average Value iv) Frequency v) Time period vi)instantaneous value after 0.05 sec.

**UNIT-III**

5. A steel ring of 180cm mean diameter has a cross-sectional area of 250mm<sup>2</sup>. Flux developed in the ring is 250μWb when a 4000 turns coil carries certain current. Calculate i) MMF required ii) Reluctance iii) current in the coil. Assume relative permeability of steel is 1100.

**OR**


6. a) Derive the expression for resonant frequency of a parallel resonant circuit.  
 b) A series RLC circuit has R=1000 , L=100mH and C=10μF. If a voltage of 100V is applied across the series combination. Calculate i) Resonant frequency ii) Q-factor and iii) Half power frequencies.

**UNIT-IV**

7. Obtain the relationship between line and phase voltages and currents in Delta connection with phasor diagram.

**OR**

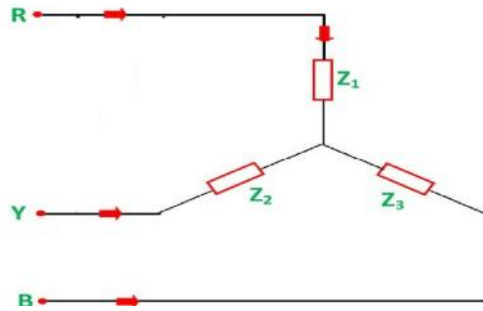8. A three phase balanced system supplies 100V, 50Hz to star connected load whose phase impedances are  $(6+j8)\Omega$ . Determine the line currents and voltages and also draw the phasor diagram.




UNIT-V

9. a) State and explain Superposition theorem with an example  
 b) State and explain Millman's theorem.

**OR**

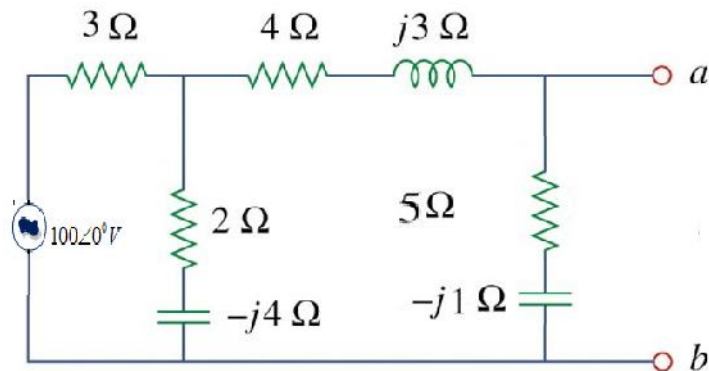10. Find the load impedance  $Z_L$  across  $ab$  for maximum power transfer to the load. Also find the max. power delivered to the load impedance for the network shown below



\*\*\*

Hall Ticket Number :									
----------------------	--	--	--	--	--	--	--	--	--

<b>R-14</b>
-------------

**Code: 4G333**

II B.Tech. I Semester Supplementary Examinations May 2019

**Signal and Systems**

( Electronics and Communication Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

<b>UNIT-I</b>
---------------

- 1. a) Obtain the condition under which two signals  $f_1(t)$  and  $f_2(t)$  are said to be orthogonal to each other. Hence prove that  $\sin n\omega_0 t$  and  $\cos m\omega_0 t$  are orthogonal to each other for all integer values of  $m, n$  7M
- b) Derive the necessary expression to represent the function  $f(t)$  using Trigonometric Fourier Series 7M

**OR**

- 2. a) Compute the Fourier Transform of i)  $f(t) = (1/2) - n u(-n-1)$  ii)  $f(t) = \sin(n/2) + \cos(n)$  8M
- b) State and prove sampling theorem for band limited signals using graphical approach. And What is aliasing? Explain its effect on sampling. 6M

<b>UNIT-II</b>
----------------

- 3. a) Find the Fourier transform of a gate pulse of unit height, unit width and centered at  $t=0$ . 7M
- b) Determine the Fourier Transform for double exponential pulse whose function is given by  $y(t) = e^{-2|t|}$  Also draw its magnitude and phase spectra 7M

**OR**

- 4. a) Find the Fourier Transform of (i) Triangular pulse with period  $T = 8\text{Sec}$  and amplitude  $A = 10\text{V}$ . (ii) One cycle of sine wave 8M
- b) What is aliasing? Explain its effect on sampling. 6M

<b>UNIT-III</b>
-----------------

- 5. a) What are the requirements of a system to allow the distortion less transmission of a signal? 7M
- b) What is the impulse response of two LTI systems connected in parallel? State the convolution Integral for CT LTI systems? 7M

**OR**

- 6. a) A stable LTI system is characterized by the differential equation  $d^2y(t)/dt^2 + 6 dy(t)/dt + 8 y(t) = 2 x(t)$  Find the frequency response & Impulse response using Fourier transform. What is the response of this system if  $x(t) = t e^{-2t} u(t)$  8M
- b) Find the impulse response of series RL circuit. What is an LTI system? Explain its properties 6M

<b>UNIT-IV</b>
----------------

- 7. a) Find the convolution of the following signals using graphical analysis:  $x(t) = e^{-2t} u(t)$  and  $h(t) = u(t + 2)$ . 7M
- b) Show that the auto-correlation function at the origin is equal to the energy of the function. 7M

OR

8. a) Show that the cross correlation of  $f(t)$  with  $(t - t_0)$  is equal to  $f(t - t_0)$ . Where  $(t - t_0)$  is delayed unit impulse function. 7M
- Prove that auto correlation function and energy/power spectral density function forms Fourier Transform pair. 7M

UNIT-V


9. a) Find the Inverse Z transform of  

$$X(z) = \frac{z+2}{4z^2 - 2z + 3} \quad |Z| < \sqrt{3/4}$$
 7M
- b) Find inverse Z-transform of  

$$X(Z) = (1 - 1/3z^{-1})(1 - 1/6z^{-1}) \quad ROC: |Z| > 1/3$$
 7M

OR

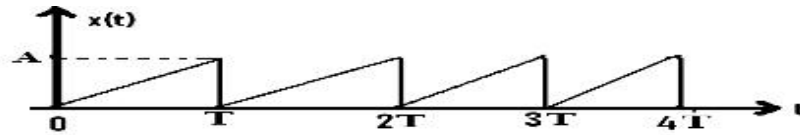- 10 a) Determine the inverse Laplace of the following functions  
 i)  $1/s(s+1)(s+3)$       ii)  $3s^2 + 8s + 6/(s+8)(s^2 + 6s + 1)$  8M
- b) Find out the Laplace transform of the signal shown in below figure. 6M



\*\*\*\*\*