

Hall Ticket Number :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

R-14

Code: 4G331

II B.Tech. I Semester Supplementary Examinations August 2021

Electronic Circuits

(Electronics and Communication Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)

UNIT-I

1. a) Compare the input impedance, output impedance and voltage gain of CE, CB and CC configurations. Why CE amplifiers are widely used? 6M
- b) Draw the circuit diagram of a two stage RC coupled amplifier. Explain the need of using multi-stage amplifiers 8M

OR

2. a) Draw and explain the circuit of cascaded amplifier and mention the advantages 7M
- b) Draw the equivalent circuit of a CE amplifier using Millers theorem. What is the upper 3-dB frequency of such circuit? 7M

UNIT-II

3. Explain the role of coupling capacitors and Bypass capacitors in a RC Coupled Amplifier Circuit. 14M

OR

4. Draw the hybrid $-\pi$ model of BJT. Explain the circuit elements in this model. 14M

UNIT-III

5. a) Explain the advantages of negative feedback over positive feedback. 7M
- b) Briefly discuss about the effect of feedback on amplifier bandwidth 7M

OR

6. a) Explain the concept of feedback with block diagram 6M
- b) Write about Classification of feedback amplifiers, 8M

UNIT-IV

7. a) With neat diagram explain about amplitude stability of oscillators. 8M
- b) Distinguish between various oscillators. 6M

OR

8. Why +ve feedback is generally used in oscillator circuits? Derive the oscillation frequency of a RC Phase Shift Oscillator. 14M

UNIT-V

9. a) Classify the power amplifiers. 7M
- b) Explain crossover distortion in Class B power amplifier 7M

OR

10. Explain in detail about complementary symmetry push pull amplifier. 14M
