

Code: 4G331

II B.Tech. I Semester Supplementary Examinations November 2019

**Electronic Circuits**

( Electronics and Communication Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

1. Explain the four h-parameters of a transistor. How these parameters are found from the characteristics of the transistor amplifier?

Show that the voltage gain of CE amplifier with an emitter resistor  $R_E$  is

$$\frac{-h_{fe}R_L}{R_S + h_{ie} + h_{fe}R_L} \text{ by assuming } h_{fe} \gg 1. \text{ Neglect } h_{re} \text{ and } h_{oe}.$$

14M


**OR**

2. Draw the equivalent circuit of a CE amplifier using Millers theorem. What is the upper 3-dB frequency of such circuit?

14M

**UNIT-II**

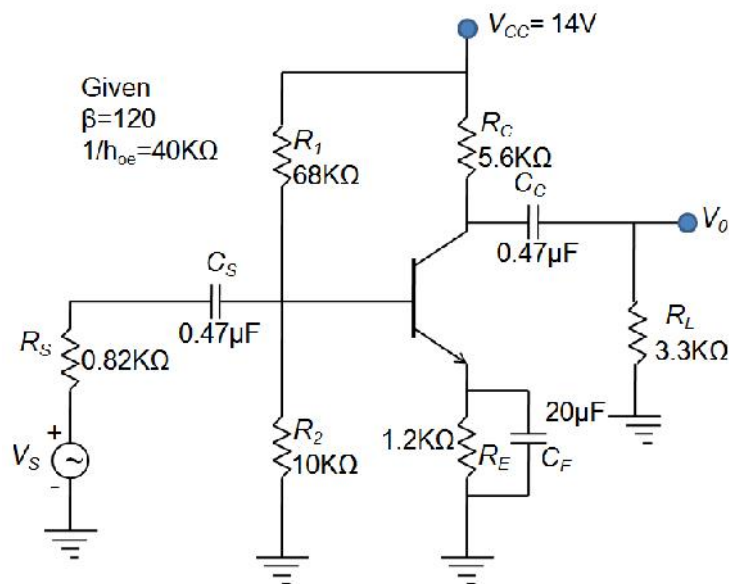3. Given  $\beta=120$ ,  $1/h_{oe}=40K\Omega$ . Obtain the cutoff frequencies associated with  $C_S$ ,  $C_C$ , and  $C_E$ .



14M

**OR**

4. Consider a single stage CE transistor amplifier with the load resistor " $R_L$ ". Find out an approximation expression for the gain factor of this amplifier.

14M


**UNIT-III**

5. Derive the input impedance ( $Z_i$ ) and output impedance ( $Z_o$ ) of a voltage series -ve feedback amplifier in terms of its open loop parameters.

14M

OR

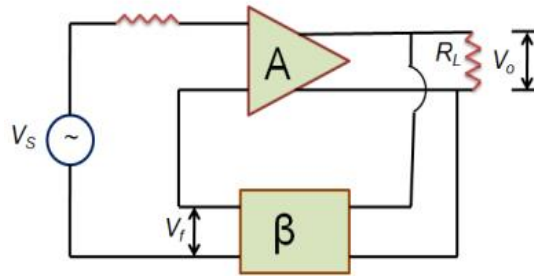6. What are the advantages of providing negative feedback to an amplifier? A series shunt feedback amplifier represented by figure using a basic voltage amplifier operates with  $V_s=100\text{mV}$  and  $V_o=10\text{V}$ . What are the values of  $A$  and  $\beta$  ?



14M

## UNIT-IV

7. Why +ve feedback is generally used in oscillator circuits? Derive the oscillation frequency of a RC Phase Shift Oscillator.

14M

OR

8. What are the primary requirements to obtain steady oscillation at a fixed frequency? Sketch the topology of a generalized resonant circuit oscillator, using impedance  $Z_1, Z_2, Z_3$ . Reduce this circuit to Hartley and Colpitts oscillator choosing components suitably? At what frequency will this circuit oscillate?

14M

## UNIT-V

9. Explain the working principle of a push pull power amplifier. Justify your answer mathematically


For a class-B Power Amplifier providing a 22V Peak signal to an 8  $\Omega$  load and a power supply of  $V_{CC}=25\text{V}$ . determine:

- Input Power,  $P_i(\text{dc})$
- Output Power,  $P_o(\text{ac})$  and
- Circuit efficiency, % .

14M

OR

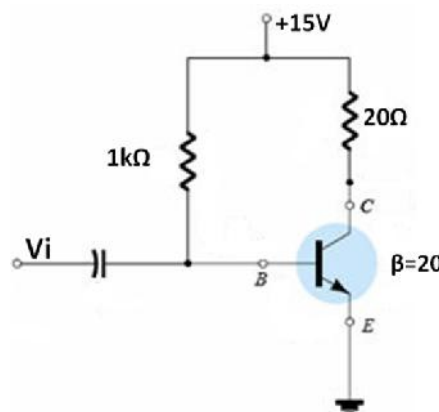10. a) Derive the maximum efficiency of a series fed class A Power amplifier.  
b) For the circuit shown, calculate the input power, the output power and efficiency of the amplifier for an input voltage resulting in a base current of 10mA peak.



14M

\*\*\*\*\*

**Code: 4G333**

II B.Tech. I Semester Supplementary Examinations November 2019

**Signals and Systems**

( Electronics and Communication Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )


\*\*\*\*\*

**UNIT-I**

- 1. a) Explain how a function can be approximated by a set of orthogonal functions. 6M
- b) State and prove any four properties of Fourier Series 8M

**OR**

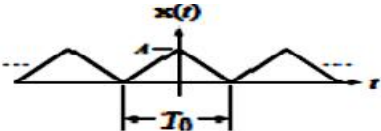- 2. a) A rectangular function  $f(t)$  is defined by  $f(t) = 1$  for  $0 < t < 1$  and  $-1$  for  $1 < t < 2$ . Approximate this function by a waveform  $\sin t$  over the interval  $(0, 2)$  such that the mean square error is minimum 7M
- b) Obtain the trigonometric Fourier series for the signal  $x(t)$



**UNIT-II**

- 3. a) State and prove Differentiation and integration properties of Fourier Transform. 7M
- b) Discuss about Hilbert transform with required equations 7M

**OR**

- 4. a) Analyze how Fourier transform is derived from Fourier series. 7M
- b) State and prove time convolution and time differentiation properties of Fourier Transform. 7M

**UNIT-III**

- 5. a) State and derive the relationship between bandwidth and rise time. 7M
- b) Discuss about distortion less transmission to a system with an example. 7M

**OR**

- 6. a) State and prove sampling theorem for band limited signals using graphical approach. 7M
- b) Determine output of an LTI system whose input and unit sample response are given as follows:  $x(n) = b^n u(n)$  and  $h(n) = a^n u(n)$ . 7M

**UNIT-IV**

- 7. a) Determine the cross correlation between the two sequences  $x(n) = \{1,0,0,1\}$  and  $h(n) = \{4,3,2,1\}$  7M
- b) Graphically convolve the signals



$$X_1(t) = \begin{cases} 1 & \text{for } -T \leq t \leq T \\ 0 & \text{else where} \end{cases} \quad \text{and}$$

$$X_2(t) = \begin{cases} 1 & \text{for } -2T \leq t \leq 2T \\ 0 & \text{else where} \end{cases}$$

7M

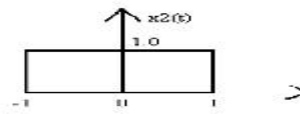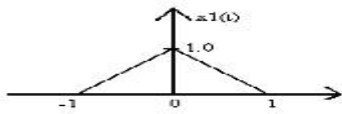**OR**

- 8 a) A system with impulse response  $e^{-t} u(t)$  is excited by a signal  $x(t) = e^{-2t} u(t)$ . Find the output of the system using convolution in time property of Fourier transform. 7M
- b) Find the Cross correlation between triangular and gate function as shown in below figure.



7M

UNIT-V

- 9 a) Find the inverse z-transform of  $x(z) = (z^2 + z)/(z - 1)(z - 3)$ , ROC:  $z > 3$  using  
i) Partial fraction method, ii) Residue method 7M
- b) State and prove initial value and final value theorems of Laplace transform 7M
- OR**
- 10 a) Find the inverse z-transform of  $x(z) = (z^2 + z)/(z - 1)(z - 3)$ , ROC:  $z > 3$  using  
i) Partial fraction method, ii) Residue method and iii) Convolution method 9M
- b) Find the inverse Laplace transform of  $F(s) = (s + 4) / (s + 3)(s + 2)$ ;  $-3 < \text{Re}(s) < -2$ . 5M

\*\*\*\*