

Hall Ticket Number :																			
----------------------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**R-14**

**Code: 4G132**

II B.Tech. I Semester Supplementary Examinations October 2020

**Digital Logic Design**

( Computer Science and Engineering )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

- 1. a) Convert the given Binary number 11011101 into
  - i. BCD
  - ii. Hexa-decimal
  - iii. Decimal
- b) Convert the hexadecimal number 68BE to binary

**OR**

- 2. a) Express the following function as a sum of minterms and as a product of maxterms:  
 $F(A,B,C,D)=B'D+A'D+BD$
- b) Implement the Boolean function  $F=xy+x'y+y'z$ 
  - i) With OR and inverter gates
  - ii) With AND and inverter gates

**UNIT-II**

- 3. a) Explain about Exclusive-OR function with an example.
- b) Explain in detail about Don't care conditions with an example.

**OR**

- 4. Explain about the Four-variable map method and simplify the Boolean function  
 $F(w,x,y,z)= (0,2,4,5,6,7,8,10,13,15)$

**UNIT-III**

- 5. a) Write down the Analysis procedure of a Combinational circuit.
- b) Explain about Binary Adder with a neat sketch.

**OR**

- 6. a) Explain about Binary Multiplier with a neat sketch.
- b) What is a Multiplexer? Explain how a Boolean function is implemented using Multiplexers.

**UNIT-IV**

- 7. a) What is flip – flop and Explain about flip- flops?
- b) Explain about shift registers?

**OR**

- 8. a) Implement JK Flip-Flop with NAND Gate
- b) Compare combinational circuit and sequential circuit

**UNIT-V**

- 9. Explain
  - (i) Circuits with latches
  - (ii) Hazards

**OR**

- 10. Implement the following Boolean function in PAL and PLA  
 $F(A,B,C)= (0,1,2,4)$

\*\*\*

Hall Ticket Number :																			
----------------------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**R-14**

**Code: 4G236**

II B.Tech. I Semester Supplementary Examinations October 2020

**Electrical Engineering and Electronics Engineering**

( Common to ME, CSE & IT )

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

- 1. a) Define the terms  
i) Electric Current ii) Potential Difference iii) Electric Power iv) Energy
- b) Three capacitors of 2 mF, 5 mF and 10 mF are connected in series. Find the equivalent capacitance.

**OR**

- 2. a) Define the Ohm's Law and its applications.
- b) State and explain Kirchoff's laws using neat diagrams.

**UNIT-II**

- 3. a) Explain the operation of principle of DC generator.
- b) Derive the expression for Torque in a DC Motor.

**OR**

- 4. a) Derive the emf equation of DC generator.
- b) A 4-pole, lap wound, DC generator has a useful flux of 0.07Wb per pole, armature consists of 440 numbers of conductors. Calculate the generated emf when it is rotated at a speed of 900 rpm with the help of prime mover.

**UNIT-III**

- 5. a) Explain the principle of operation of single phase Transformer with neat sketch.
- b) Explain Torque-Slip Characteristics of a Three phase induction motor.

**OR**

- 6. a) Derive the expression for E.M.F equation of a transformer.
- b) Explain the principle operation of a three phase induction motor with relevant diagrams

**UNIT-IV**

- 7. Explain the operation of Half wave rectifier with relevant diagrams.

**OR**

- 8. a) Explain the operation of P-N junction diode mentioning its applications.
- b) Explain the input and output characteristics of transistor in CE configuration.

**UNIT-V**

- 9. Describe how phase and frequency are measured by using Lissajous figures.

**OR**

- 10. a) Describe how voltage, current and time period are measured by using CRO.
- b) List the applications of CRO.

\*\*\*