

Hall Ticket Number :									
----------------------	--	--	--	--	--	--	--	--	--

R-14

Code: 4G236

II B.Tech. I Semester Supplementary Examinations November 2019

Electrical Engineering and Electronics Engineering

(Common to ME, CSE & IT)

Max. Marks: 70

Time: 3 Hours

Answer all five units by choosing one question from each unit (5 x 14 = 70 Marks)

UNIT-I

1. a) Define the Ohm's Law and its applications. 7M
- b) State and explain Kirchoff's laws using neat diagrams. 7M

OR

2. a) Derive the expression for delta to star transformation. 7M
- b) Two resistances of 1.5 and 3.5 are connected in parallel and their combination is connected in series with a resistance of 1.95. Find the equivalent resistance of the circuit. What current will it draw if connected to a 30V supply? 7M

UNIT-II

3. a) A 6 pole, lap wound armature has 840 conductors and flux per pole of 0.018wb. Calculate the emf generated when the machine is running at 600rpm. 7M
- b) Explain the operation & principle of dc motors and explain the significance of back emf in dc motors. 7M

OR

4. Explain classification of a DC generator along with suitable diagrams and voltage and current relationship. 14M

UNIT-III

5. a) Derive the expression for E.M.F equation of a transformer. 7M
- b) Explain the principle operation of a three phase induction motor with relevant diagrams 7M

OR

6. a) Describe the tests that can be performed on a single phase transformer in detail. 7M
- b) A 3- induction motor runs at 1200 rpm at no load and 1140 rpm at full load when supplied with power from a 60Hz, 3 phase line. Calculate number of poles and slip at full load. 7M

UNIT-IV

7. Explain the operation of Half wave rectifier with relevant diagrams. 14M

OR

8. a) Construct the practical circuit of a transistor and elaborate it. 7M
- b) Explain the operation of transistor as an amplifier. 7M

UNIT-V

9. Describe how phase and frequency are measured by using Lissajous figures. 14M

OR

10. Explain the Block diagram of CRO with a neat sketch. 14M
