

|                      |  |  |  |  |  |  |  |  |  |
|----------------------|--|--|--|--|--|--|--|--|--|
| Hall Ticket Number : |  |  |  |  |  |  |  |  |  |
|----------------------|--|--|--|--|--|--|--|--|--|

|             |
|-------------|
| <b>R-17</b> |
|-------------|

**Code: 7G334**

II B.Tech. I Semester Supplementary Examinations November 2023

**Analog Electronics - I**

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

1. Draw and discuss the Frequency response of RC Coupled, Direct coupled and Transformer coupled amplifiers with relevant diagrams. 14M

**OR**

2. a) Distinguish between Exact and approximate models of BJT using h-parameters. 5M  
b) State and prove millers theorem. Explain its significance in transistor circuit analysis. 9M

**UNIT-II**

3. a) Derive the expression for transfer gain with feedback? 7M  
b) What is Sampling. Explain about it with neat diagrams. 7M

**OR**

4. a) An amplifier has an open loop gain 1000 and a feedback ratio of 0.04. if the open loop gain changed by 10% due to temperature, then find the percentage change in gain of the amplifier with feedback. 7M  
b) Derive the expressions for input impedance, output impedance for current series feedback. 7M

**UNIT-III**

5. a) Explain about the crystal oscillators and mention their advantages 7M  
b) Write short notes on Frequency stability of oscillators 7M

**OR**

6. a) Discuss about Hartley oscillator with the help of circuit diagram. 10M  
b) Determine the Resistance of RC phase shift oscillator for operation at  $f_o = 10 \text{ KHz}$ ,  $K=45$  and  $C= 2\text{pF}$ . 4M

**UNIT-IV**

7. a) Write short notes on Class-A direct coupled Class-A power amplifier. 7M  
b) Explain class A power amplifier working with neat sketches and derive the expression for conversion efficiency. 7M

**OR**

8. a) Derive the expression for efficiency in class B amplifier 7M  
b) What is the Max power dissipation per each transistor and derive the expression for it. 7M

**UNIT-V**

9. a) What is RC low-pass circuit? What is meant by ringing circuit? 7M  
b) Explain the RC Integrator with Exponential input. 7M

**OR**

10. a) Discuss about transistor clippers. 7M  
b) State and prove clamping circuit theorem. 7M

\*\*\*

Hall Ticket Number : 

|  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|

**R-17**

**Code: 7GC32**

II B.Tech. I Semester Supplementary Examinations November 2023

**Engineering Mathematics-III**

(Common to All Branches)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks )

\*\*\*\*\*

Marks

**UNIT-I**

1. a) Find the real root of equation  $x^3 - x - 11 = 0$  by bisection method. 7M
- b) Using Taylor's series method, compute the value of  $y$  at  $x=0.2$  from  $\frac{dy}{dx} = x + y$ ;  $y(0) = 1$ . 7M

**OR**

2. Using R-K method of 4<sup>th</sup> order, solve  $\frac{dy}{dx} = \frac{y^2 - x^2}{y^2 + x^2}$ ,  $y(0) = 1$ . Find  $y(0.2)$ ,  $y(0.4)$ . 14M

**UNIT-II**

3. a) Find the first and second derivatives of the function tabulated below at the point  $x = 1.5$
- |   |       |     |        |      |        |      |
|---|-------|-----|--------|------|--------|------|
| x | 1.5   | 2.0 | 2.5    | 3.0  | 3.5    | 4.0  |
| y | 3.375 | 7.0 | 13.625 | 24.0 | 38.875 | 59.0 |
- 7M
- b) Evaluate  $f(10)$  given  $f(x) = 168, 192, 336$  at  $x = 1, 7, 15$  respectively. Use Lagrange interpolation. 7M

**OR**

4. A solid of revolution is formed by rotating about the x-axis, the area between the x-axis, the lines  $x=0$  and  $x=1$  and a curve through the points with the following co-ordinates:
- |   |        |        |        |        |        |
|---|--------|--------|--------|--------|--------|
| x | 0.00   | 0.25   | 0.5    | 0.75   | 1.00   |
| y | 1.0000 | 0.9896 | 0.9589 | 0.9089 | 0.8415 |
- Estimate the volume of the solid formed using Simpsons rule. 7M

**UNIT-III**

5. a) Form the partial differential equation by eliminating the arbitrary constants  $x^2 + y^2 + (z - c)^2 = a^2$  7M
- b) Fit a second degree parabola to the following data by the method of least squares
- |   |    |    |    |    |    |
|---|----|----|----|----|----|
| x | 10 | 12 | 15 | 23 | 20 |
| y | 14 | 17 | 23 | 25 | 21 |
- 7M

**OR**

6. a) Fit a straight line  $y = a + bx$  to the data by the method of least squares
- |   |   |   |   |   |   |
|---|---|---|---|---|---|
| x | 0 | 1 | 3 | 6 | 8 |
| y | 1 | 3 | 2 | 5 | 4 |
- 7M
- b) Form the partial differential equation by eliminating  $a, b$  from  $z = ax + by + a^2 + b^2$  7M

Important Note: 1. On completing your answers. Compulsorily draw diagonal cross line on the remaining blank pages. 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 32+8=40, will be treated as malpractice.

|                |
|----------------|
| <b>UNIT-IV</b> |
|----------------|

7. a) Find the Fourier series expansion for  $f(x) = f - x$  in  $0 < x < 2f$  7M  
 b) Expand  $f(x) = \cos x, 0 < x < f$  in half range sine series. 7M

**OR**

8. Express  $f(x) = x$  as half range sine and cosine in  $0 < x < 2$  14M

|               |
|---------------|
| <b>UNIT-V</b> |
|---------------|

9. a) Find the Fourier sin and cosine transform of  $f(x) = \frac{e^{-ax}}{x}, a > 0$  7M  
 b) Find the Fourier cosine transform of  $f(x) = e^{-ax} (x > 0, a > 0)$ . 7M

**OR**

10. Find the Fourier transform of  $f(x) = \begin{cases} 1-x^2, & |x| \leq 1 \\ 0, & |x| \geq 1 \end{cases}$ .

Hence evaluate  $\int_0^{\infty} \frac{x \cos x - \sin x}{x^3} \cos \frac{x}{2} dx$

14M

\*\*\*