

Hall Ticket Number :

R-20

Code: 20A432T

II B.Tech. I Semester Supplementary Examinations July 2023

Digital Logic Design

(Electronics and Communication Engineering)

Max. Marks: 70

Time: 3 Hours

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
2. In Part-A, each question carries **Two marks**.
3. Answer **ALL** the questions in **Part-A** and **Part-B**

PART-A

(Compulsory question)

1. Answer **all** the following short answer questions (5 X 2 = 10M)
- | | | |
|---|-----|----|
| | CO | BL |
| a) Determine the value of base x if $(211)_x = (152)_8$ | CO1 | L1 |
| b) Design 2x4 decoder using NAND gates | CO2 | L3 |
| c) Write the differences between the Combinational and sequential circuits. | CO3 | L2 |
| d) What are the classifications of sequential circuits? | CO3 | L1 |
| e) Define state and state diagram. | CO4 | L1 |

PART-B

Answer five questions by choosing one question from each unit (5 x 12 = 60 Marks)

Marks CO BL

UNIT-I

2. a) Subtract the following decimal numbers by the 9's and 10's complement methods. i) 93 - 615 ii) 574.6 - 297.7 iii) 376.3 - 765.6
- | | | | |
|--|----|-----|----|
| | 6M | CO1 | L2 |
|--|----|-----|----|
- b) Reduce the following Boolean function to three literals and draw the logic diagram: $(x'y'+z)'+z+xy+wz$.
- | | | | |
|--|----|-----|----|
| | 6M | CO1 | L2 |
|--|----|-----|----|

OR

3. a) A 12 bit Hamming code word containing 8 bits of data and 4 parity bits is read from memory. What was the original 8 bit data word that was written into memory if the 12 bit word read out is as 101110010100?
- | | | | |
|--|----|-----|----|
| | 6M | CO1 | L3 |
|--|----|-----|----|
- b) Write a brief note on Gray codes. Also discuss methods for conversion from gray to binary code and vice versa.
- | | | | |
|--|----|-----|----|
| | 6M | CO1 | L2 |
|--|----|-----|----|

UNIT-II

4. a) Rewrite the following Boolean expression in the minterm and maxterm canonical and Standard forms. $f(x,y,z) = x'(y'+z)+z'$
- | | | | |
|--|----|-----|----|
| | 6M | CO2 | L2 |
|--|----|-----|----|
- b) Using K-map find the minimized Boolean function and its complement for the following $f(A,B,C,D) = m(1,2,3,4,6,8,9,10,11,12,14)$.
- | | | | |
|--|----|-----|----|
| | 6M | CO2 | L3 |
|--|----|-----|----|

OR

5. a) Simplify the following Boolean function using tabular method:
 $f(A, B, C, D) = m(0, 6, 8, 13, 14) + d(2, 4, 10)$ and identify essential prime implicants.
- | | | | |
|--|----|-----|----|
| | 6M | CO2 | L3 |
|--|----|-----|----|
- b) A truth table has four inputs variables. The first eight outputs are 0's and the last eight output are 1's. Draw the k-Map and write down the simplified expression
- | | | | |
|--|----|-----|----|
| | 6M | CO2 | L3 |
|--|----|-----|----|

UNIT-III

6. a) Realize the following Boolean function with multiplexer
 $f(A,B,C,D) = m(0,1,3,4,8,9,15)$.
 i) Using 8:1 MUX with A,B,C select lines
 ii) Using 4:1 MUX with A,B select lines
- b) Design a digital system to add two Binary Coded Decimal numbers using binary adder.

6M CO3 L3

6M CO3 L3

OR

CO3

7. a) Implement 4*16 decoder using two 3*8 decoders.
 b) Give circuit implementation of 4 Bit Ripple Adder/Subtractor using twos complement method.

6M CO3 L3

6M CO3 L2

UNIT-IV

8. a) With the help of logic diagram, explain working of Master slave JK Flip-Flop along with waveforms. Explain race around condition. How is it eliminated?
 b) Convert JK Flip-Flop to SR Flip-Flop.

6M CO3 L2

6M CO3 L2

OR


9. a) Design a D type positive edge triggered flip-flop. Explain the operation of the sequential circuit when CP = 1.
 b) Design a 4-bit Johnson counter and explain.

6M CO3 L3

6M CO3 L3

UNIT-V

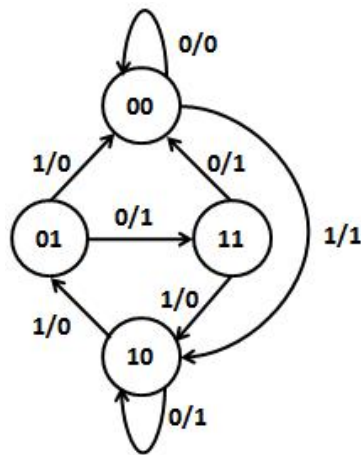10. Construct a sequential logic circuit with single input and single output by obtaining the state and excitation table for the given state diagram using JK FF.



12M CO4 L3

OR

11. Construct Moore and Mealy state diagram that will detect input sequence 10110, when input pattern is detected, z is asserted high. Give state diagram for each state.

12M CO4 L3

*** End ***

Hall Ticket Number :

R-20

Code: 20AC36T

II B.Tech. I Semester Supplementary Examinations July 2023

Managerial Economics and Financial Analysis

(Common to CE & ECE)

Max. Marks: 70

Time: 3 Hours

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)

2. In Part-A, each question carries **Two marks**.

3. Answer **ALL** the questions in **Part-A** and **Part-B**

PART-A

(Compulsory question)

- | | | |
|---|-----|----|
| 1. Answer all the following short answer questions (5 X 2 = 10M) | CO | BL |
| a) State the law of demand. | CO1 | L2 |
| b) Write a short note on Isoquants. | CO2 | L1 |
| c) What is joint Hindu family business? | CO3 | L1 |
| d) List the methods of capital budgeting. | CO4 | L3 |
| e) Differentiate tangible assets from intangible assets. | CO5 | L1 |

PART-B

Answer **five** questions by choosing one question from each unit (5 x 12 = 60 Marks)

Marks CO BL

UNIT-I

- | | | | |
|--|-----|-----|----|
| 2. Explain the reasons why demand curve always slopes downwards. | 12M | CO1 | L2 |
|--|-----|-----|----|

OR

- | | | | |
|---|-----|-----|----|
| 3. What are the various forecasting techniques? Explain each of them in detail. | 12M | CO1 | L2 |
|---|-----|-----|----|

UNIT-II

- | | | | |
|--|-----|-----|----|
| 4. Explain the behavior of Total Cost (TC), Total Variable Cost (TVC) and Total Fixed Cost using suitable cost-output diagram. | 12M | CO2 | L4 |
|--|-----|-----|----|

OR

- | | | | |
|--|-----|-----|----|
| 5. From the following information calculate the breakeven point and the turnover required to earn a profit of Rs.36,000. Given that
Fixed overheads-Rs.1,80,000
Variable cost per unit-Rs.2/ and Selling price-Rs.20/.
If the company is earning a profit of Rs.36, 000, find the margin of safety available to it. | 12M | CO2 | L1 |
|--|-----|-----|----|

UNIT-III

- | | | | |
|---|-----|-----|----|
| 6. Explain the price output decision under monopolistic competition in the long run with the help of diagram. | 12M | CO3 | L1 |
|---|-----|-----|----|

OR

7. Summarize the differences between private company and public company. 12M CO3 L1

UNIT-IV

8. Discuss the different sources of raising capital, for an organization. 12M CO4 L1

OR

9. Compute the NPV for the projects X and Y and choose the best. The firm's cost of capital is 10%.

Year	Project X	Project Y
0	70,000	70,000
1	10,000	50,000
2	20,000	40,000
3	30,000	20,000
4	45,000	10,000
5	60,000	10,000

12M CO4 L4

UNIT-V

10. a) Discuss the importance of financial statement analysis in business. 6M CO5 L3
- b) Summarize the managerial applications of ratio analysis. 6M CO5 L3

OR

11. Journalize the following entries in the Books of M/s. Rock Well Industries Ltd.

No	Date	Description	Rs. Lakhs
1	01-05-2020	Started Business with cash	5.00
2	02-05-2020	Deposited in Andhra Bank	3.00
3	05-05-2020	Purchased Goods on Credit from ABC Ltd	15.00
4	08-05-2020	Sold goods on Credit to XYZ Ltd	5.00
5	10-05-2020	Paid Freight Charges by Cheque	0.25
6	25-05-2020	Paid Salaries from Bank	2.00
7	30-05-2020	Drawn Cash from Bank	5.00
8	31-05-2020	Purchased Furniture on Credit from GBL	1.20

12M CO5 L3

*** End ***.

Hall Ticket Number :									
----------------------	--	--	--	--	--	--	--	--	--

R-20

Code: 20A431T

II B.Tech. I Semester Supplementary Examinations July 2023

Signals & Systems

(Electronics and Communication Engineering)

Max. Marks: 70

Time: 3 Hours

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. In Part-A, each question carries **Two marks**.
 3. Answer **ALL** the questions in **Part-A** and **Part-B**

PART-A

(Compulsory question)

- | | | |
|---|-----|----|
| 1. Answer all the following short answer questions (5 X 2 = 10M) | CO | BL |
| a) Sketch the following signal: $y(t) = r(t) - r(t-2) - r(t-3) + r(t-4)$ | CO1 | L1 |
| b) Determine the Fourier transform of Signum function. | CO2 | L2 |
| c) Determine the Nyquist sampling rate and Nyquist sampling interval for the signal: $x(t) = \text{sinc}(100t) + 5 \text{sinc}^2(200t)$ | CO3 | L2 |
| d) Compare ESD and PSD. | CO4 | L2 |
| e) State the properties of ROCs of X(z). | CO5 | L2 |

PART-B

Answer **five** questions by choosing one question from each unit (5 x 12 = 60 Marks)

Marks CO BL

UNIT-I

- | | | | |
|---|----|-----|----|
| 2. a) Determine whether the following system is Linear or non-linear
$\frac{d^3y(t)}{dt^3} + 5 \frac{d^2y(t)}{dt^2} + 6 \frac{dy(t)}{dt} + 2y(t) = x^2(t)$ | 6M | CO1 | L2 |
| b) Obtain the exponential Fourier series for the function $x(t) = A \sin(t)$ over the interval $0 \leq t \leq \pi$. | 6M | CO1 | L2 |

OR

- | | | | |
|--|----|-----|----|
| 3. a) Derive the expressions for the trigonometric Fourier series coefficients. | 6M | CO1 | L2 |
| b) Find the trigonometric Fourier series of $x(t) = t^2$ over the interval (-1,1). | 6M | CO1 | L3 |

UNIT-II

- | | | | |
|---|----|-----|----|
| 4. a) Compute the Fourier transform of the following signals
i) $e^{-at}u(t)$ ii) Triangular pulse | 6M | CO2 | L4 |
| b) For a signal x(t), the FT is X(f). Determine the Inverse FT of X(3f+2). | 6M | CO2 | L2 |

OR

5. a) State and prove the following properties of Fourier series.
 (i). time shifting (ii). convolution 6M CO2 L2
 b) What is Hilbert transform? How does it differ from other transforms? 6M CO2 L1

UNIT-III

6. a) State and prove the properties of LTI Systems 6M CO3 L2
 b) Obtain the conditions for the Distortionless transmission through a system. 6M CO3 L2

OR

7. a) State and prove sampling theorem for low pass signals. 8M CO3 L2
 b) The spectral range of a signal extends from 5.6 MHz to 6.8 MHz. Find the minimum sampling rate and maximum sampling time. 4M CO3 L2

UNIT-IV

8. a) For a system excited by $x(t) = e^{-2t}u(t) + e^{-3t}u(-t)$, find the impulse response $h(t)$ and the output for the system. 6M CO4 L2
 b) Show that the convolution of two odd functions is an even function. 6M CO4 L2

OR

9. a) Show that auto correlation function and ESD form a Fourier transform pair. 6M CO4 L2
 b) Find the autocorrelation and ESD of signal $x(t) = e^{-t}u(t)$ using the relation between convolution and correlation. 6M CO4 L2

UNIT-V

10. a) State and prove any two properties of Laplace transforms. 6M CO5 L2
 b) If $X(s) = \frac{s+2}{s^2+8s+25}$, find $x(t)$, $t \geq 0$. 6M CO5 L2

OR

11. a) Prove that the sequence $x(n) = a^n u(n)$ and $x(n) = -a^n u(-n-1)$ have the same $X(z)$ and differ only in ROC. 6M CO5 L3
 b) Find the Inverse Z-transform of the sequence $X(Z) = \frac{z}{2z^2 - 3z + 1}$, ROC: $|z| > 1$ 6M CO5 L2

*** End ***

Hall Ticket Number :									
----------------------	--	--	--	--	--	--	--	--	--

R-20

Code: 20AC32T

II B.Tech. I Semester Supplementary Examinations July 2023

Transform Techniques & Complex Variables

(Common to EEE and ECE)

Max. Marks: 70

Time: 3 Hours

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. In Part-A, each question carries **Two marks**.
 3. Answer **ALL** the questions in **Part-A** and **Part-B**

PART-A

(Compulsory question)

- | | | |
|--|----|----|
| 1. Answer <i>all</i> the following short answer questions (5 X 2 = 10M) | CO | BL |
| a) Answer <i>all</i> the following short answer questions (5 X 2 = 10M) | | |
| What is unit step function and write Laplace transform of unit step function $u(t - a)$. State convolution theorem. | 2 | 2 |
| b) State convolution theorem. | 2 | 1 |
| c) Define half- range sine series, half-range cosine series. | 2 | 1 |
| d) Find real and imaginary parts of $f(z) = \frac{z^2 - 2z + 1}{z^2 + 1}$. | 2 | 2 |
| e) Find the poles and order of poles of $f(z) = \frac{z}{z^2 + 1}$. | 2 | 2 |

PART-B

Answer *five* questions by choosing one question from each unit (5 x 12 = 60 Marks)

Marks CO BL

UNIT-I

- | | | |
|---|----|-----|
| 2. a) Find $L\left(\int_0^t e^{-t} \sin \frac{1}{t} dt\right)$ | | |
| b) Apply Laplace transform and evaluate $\int_0^c \frac{\sin 2t}{t} dt$ | | |
| | 6M | 1 2 |
| | 6M | 1 3 |

OR

- | | | |
|---|----|-----|
| 3. a) Find Laplace transform of $\cos t \cos 2t \cos 3t$. | | |
| b) Find Laplace transform of $\frac{\cos \sqrt{t}}{\sqrt{t}}$ and hence find transform of $\sin \sqrt{t}$ and $\cos \sqrt{t}$. | | |
| | 6M | 1 2 |
| | 6M | 1 3 |

UNIT-II

- | | | |
|---|----|-----|
| 4. a) Find inverse Laplace transform of $\frac{1}{\sqrt{2s-3}}$ | | |
| b) Apply convolution and find $L^{-1}\left[\frac{1}{(s^2+a^2)(s^2+b^2)}\right]$. | | |
| | 6M | 2 2 |
| | 6M | 2 3 |

OR

- | | | |
|---|----|-----|
| 5. a) Find $L^{-1}\left[\frac{2s-5}{s^2-4}\right]$ | | |
| b) Solve $x'' + 2x' + x = 3te^{-t}$ given $x(0) = 4, x'(0) = 0$ | | |
| | 6M | 2 2 |
| | 6M | 2 3 |

UNIT-III

6. a) Find Fourier series of the function $f(x) = e^{-x}$ in $(0, 2\pi)$. 6M 3 3
 b) Using Fourier sine integral show that

$$\int_0^{\infty} \frac{\sin ax \cos bx}{(a^2 + x^2)(b^2 + x^2)} dx = \frac{f}{2(b^2 - a^2)} (e^{-ax} - e^{-bx}),$$

$a, b > 0$ 6M 3 3

OR

7. a) Find the Fourier Sine transform and Fourier Cosine transform of $f(x) = 2e^{-5x} + 5e^{-2x}$. 6M 3 3
 b) Find the half range cosine series of $f(x) = (x^2 \sin x)^2$ or the interval $0 < x < \pi$ and show that $\frac{1}{12} + \frac{1}{32} + \frac{1}{52} + \dots = \frac{\pi}{8}$. 6M 3 3

UNIT-IV

8. a) Show that the function $f(z) = \sqrt{|xy|}$ is not analytic at the origin although Cauchy-Riemann equations are satisfied at that point. 6M 4 3
 b) Evaluate $\int_C (z^2 + x^2) dx + (z^2 + y^2) dy + (x^2 + y^2) dz$ from $(0, 0, 0)$ to $(1, 1, 1)$ Where C is the curve $x=t, y=t^2, z=t^3$ in the parametric form. 6M 4 3

OR

9. a) Find the analytic function $f(z) = u+iv$ if $u-v = e^x(\cos y - \sin y)$ 6M 4 3
 b) Evaluate $\int_C \frac{z^3 e^{-z}}{(z-1)^3} dz$ where C is $|z-1| = \frac{1}{2}$ using Cauchy's integral formula 6M 4 3

UNIT-V

10. a) Find the Taylor's series expansion of $f(z) = \frac{1}{z^2 + z - 6}$ in the region $|z| < 1$ 6M 5 3
 b) Apply Cauchy's residue theorem, evaluate $\int_C \frac{z-3}{z^2 + 2z + 5} dz$ where C is the circle $|z + 1 + i| = 2$. 6M 5 3

OR

11. a) Expand $f(z) = \frac{z+3}{z(z^2 - z - 2)}$ in power series of z where $1 < |z| < 2$ 6M 5 3
 b) Find the residues of $f(z) = \frac{\sin \pi z^2 + \cos \pi z^2}{(z-1)^2(z-2)}$ and evaluate $\int_C f(z) dz$ where C is $|z| = 3$. 6M 5 3

*** End ***

Hall Ticket Number :									
----------------------	--	--	--	--	--	--	--	--	--

R-20

Code: 20A433T

II B.Tech. I Semester Supplementary Examinations July 2023

Analog Circuits

(Electronics and Communication Engineering)

Max. Marks: 70

Time: 3 Hours

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. In Part-A, each question carries **Two marks**.
 3. Answer **ALL** the questions in **Part-A** and **Part-B**

PART-A

(Compulsory question)

- | | | |
|---|----|----|
| 1. Answer all the following short answer questions (5 X 2 = 10M) | CO | BL |
| a) State Miller's theorem. | 1 | 1 |
| b) List the advantages of negative feedback. | 2 | 1 |
| c) What are the primary requirements to obtain steady oscillation at a fixed frequency? | 3 | 5 |
| d) What is the maximum efficiency of class B amplifier? | 4 | 4 |
| e) Draw a Transistor clipper circuit. | 5 | 2 |

PART-B

Answer **five** questions by choosing one question from each unit (5 x 12 = 60 Marks)

Marks CO BL

UNIT-I

- | | | | |
|---|----|---|---|
| 2. a) Illustrate the h-parameter model of a BJT-CE amplifier and derive the equations for voltage gain, current gain, input impedance and output impedance. | 6M | 1 | 2 |
| b) The hybrid parameters of a transistor used as an amplifier in the CE configuration are $h_{ie} = 800$, $h_{fe}=46$, $h_{oe}=80 \times 10^{-6}$ and $h_{re}=5.4 \times 10^{-4}$. If $R_L=5k$ and $R_s =500$. Find A_i , R_i , A_v , R_o . | 6M | 1 | 4 |

OR

- | | | | |
|--|----|---|---|
| 3. a) i. Given $\beta =120$, $r_e=4.5$, and $r_o=40k$, sketch the approximate hybrid equivalent circuit. | | | |
| ii. Given $h_{ie}=1k$, $h_{re}=2 \times 10^{-4}$, $h_{fe}=90$, and $h_{oe} = 20 \mu S$, sketch the re model. | 8M | 1 | 5 |
| b) Explain dual of miller's theorem | 4M | 1 | 1 |

UNIT-II

- | | | | |
|---|----|---|---|
| 4. a) If an amplifier with gain of -1000 and feedback of $\beta =-0.1$ has a gain change of 20% due to temperature, calculate the change in gain of the feedback amplifier. | 6M | 2 | 3 |
| b) List the general characteristics of negative feedback amplifiers. | 6M | 2 | 1 |

OR

5. a) Discuss in detail about voltage-series feedback and voltage-shunt feedback amplifier. 6M 2 2
- b) Calculate the gain, input, and output impedances of a voltage-series feedback amplifier having $A_v = -300$, $R_i = 1.5 \text{ k}\Omega$, $R_o = 50 \text{ k}\Omega$, and $\beta = -1/15$. 6M 2 3

UNIT-III

6. a) Design a passive RC phase shift network to achieve a phase shift of 60° . 6M 3 5
- b) An amplifier bursts into oscillation when the loop gain $A\beta = 1$, but for sustained oscillation $A\beta > 1$. Why so? 6M 3 3

OR

7. a) Explain the principle of operation of crystal oscillator. Draw the frequency response of crystal oscillator. 6M 3 4
- b) A 1 mH inductor is available. Choose the capacitor values in a Colpitts oscillator so that $f = 1 \text{ MHz}$ and $Q = 0.25$. 6M 3 3

UNIT-IV


8. a) For a class B amplifier providing a 20 V peak signal to a 16Ω load (speaker) and a power supply of $V_{CC} = 30 \text{ V}$, determine the input power, output power, and circuit efficiency. 6M 4 5
- b) With suitable circuit diagram explain a class A amplifier. 6M 4 2

OR

9. a) With suitable circuit diagram explain a push-pull amplifier. 6M 4 1
- b) Explain power dissipation in transistor amplifier. Suggest the methods to address this issue. 6M 4 5

UNIT-V

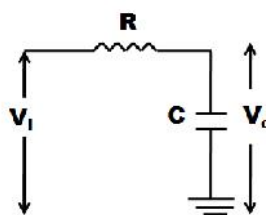
10. a) Find out the impulse response of a single stage low pass filter. 6M 5 4
- b) Compute the time domain output of this circuit of a power of 1 volt is given as its input.



6M 5 5

OR

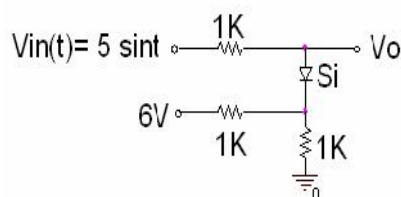11. a) Determine the output for the following circuits



6M 5 3

- b) State and prove clamping circuit theorem. 6M 5 4

*** End ***