

Hall Ticket Number :

R-17**Code: 7G345**

II B.Tech. II Semester Regular & Supplementary Examinations November 2020

Analog Electronics-II

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five questions from the following (5 x 14 = 70 Marks)

		Marks	CO	BL
1.	a) Define an IC and give the classification of IC's in detail.	7M	1	1
	b) Discuss the AC characteristics of an Op Amp	7M	1	2
2.	a) Describe the internal block diagram of an Op-amp and explain each block in detail	7M	1	2
	b) Draw the ideal characteristics of an op-amp and draw its block diagram.	7M	1	1
3.	a) In an inverting adder circuit, the input voltages are 0.3V, 0.5V, 0.1V while $R_1=R_2=R_3=1\text{ K}$, $R_f=10\text{K}$. Calculate the output voltage.	7M	2	3
	b) Evaluate and derive an expression for V_o of the practical differentiator circuit by using op amp.	7M	2	6
4.	a) Evaluate the time period of a free running astable multivibrator used as square wave generator using op-amp.	7M	2	6
	b) Explain the working and operation of anti log amplifier using op-amp.	7M	2	2
5.	a) Explain the working of a comparator using op amp. What are its limitations?	7M	2	2
	b) Discuss in detail about the operation of sawtooth wave generator using op-amp.	7M	2	2
6.	a) Realize a monostable multivibrator using 555 timer to obtain pulse of width of 0.1msec. Draw the circuit diagram with its waveforms.	7M	4	4
	b) Realize the Schmitt trigger using a 555 timer IC.	7M	4	4
7.	a) Draw and explain the principle of operation of dual slope ADC.	7M	5	2
	b) A 12-bit D to A convertor has a full-scale range of 15 volts. Its maximum differential linearity error is $\pm 1/2$ LSB.			
	i) What is the percentage resolution			
	ii) What are the minimum and maximum possible values of the increment in its output voltage?	7M	5	3
8.	a) Explain the working of a successive approximation ADC with neat sketches.	7M	5	1
	b) Explain the operation of an R-2R ladder DAC and mention its applications.	7M	5	3

Code: 7GC43

II B.Tech. II Semester Regular & Supplementary Examinations November 2020

Complex Variables and Special Functions

(Common to EEE & ECE)

Max. Marks: 70

Time: 3 Hours

Answer any five questions from the following (5 x 14 = 70 Marks)

- | | Marks | CO | Blooms Level |
|--|-------|----|--------------|
| 1. a) Show that $\beta(m, n) = \frac{\Gamma(m)\Gamma(n)}{\Gamma(m+n)}$, $m > 0, n > 0$. | 7M | 2 | II |
| b) Find the general and principal values of $\log(1 + i\sqrt{3})$. | 7M | 2 | I |
| 2. a) Show that $\beta(m, \frac{1}{2}) = 2^{2m-1} \beta(m, m)$. | 7M | 2 | II |
| b) If $\tan(x + iy) = A + iB$ then show that $A^2 + B^2 + 1 = 0$. | 7M | 2 | II |
| 3. a) If $w = \log z$, find $\frac{dw}{dz}$ and describe where w is non-analytic. | 7M | 1 | I |
| b) Show that $(\frac{\partial^2}{\partial x^2} + \frac{\partial^2}{\partial y^2}) \log f'(z) = 0$ where $f(z)$ is an analytic function. | 7M | 1 | I |
| 4. a) Evaluate $\int_C \bar{z} dz$ from $z = 1$ to $z = 1 + 2i$ along the curve $C: x = t^2, y = t$. | 7M | 2 | V |
| b) Express $\int_C \bar{z} dz$ as a series in the region $0 < z < 1$. | 7M | 2 | II |
| 5. a) Show that $\int_C e^{-2z} dz$ is independent of the path C' joining the points $1 - \pi i$ and $2 + 3\pi i$. Determine its value. | 7M | 2 | II |
| b) Find the Taylor's series expansion of e^z about $z = 1$. | 7M | 2 | I |
| 6. Evaluate $\int_0^{2\pi} \frac{d\theta}{17 - 8 \cos \theta}$ by contour integration applying the calculus of residues. | 14M | 3 | V |
| 7. a) Show that the function $w = \frac{4}{z} \tan^{-1} z$ transforms the straight line $x = c$ in the z -plane into a circle in the w -plane. | 7M | 2 | II |
| b) Find the bilinear transformation which maps the points $1, i, -1$ onto the points $w = i, 0, -i$. | 7M | 2 | I |
| 8. a) Show that the relation $w = \frac{5-4z}{4z-2}$ transforms the circle $ z = 1$ into a circle of radius unity in the w -plane. | 7M | 2 | II |
| b) Find the bilinear transformation which maps the points $(-1, 0, 1)$ into the points $(0, i, 3i)$. | 7M | 2 | I |

Code: 7G244

II B.Tech. II Semester Regular & Supplementary Examinations November 2020

Electrical Circuits-II

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five questions from the following (5 x 14 = 70 Marks)

- | | Marks | CO | Blooms Level |
|---|-------|----|--------------|
| 1. a) A single phase three wire system is fed by $V_{an} = V_{nb} = 100 \angle 0^\circ$ V rms. The two outside line currents are $I_{aA} = 10 + j0$ and $I_{bB} = -9 + j1$ A rms. If load $Z_{AN} = 20 + j0$. Find Z_{BN} and Z_{AB} . Assume zero line resistance | 7M | 1 | I |
| b) Explain the power measurement in a three phase circuit using two wattmeter method | 7M | 1 | II |
| 2. a) Find the inverse Laplace transform for the following function
(i) $s / (s+3)$
(ii) $\ln \left[\frac{s+1}{s+3} \right]$ | 7M | 2 | I |
| b) Find the both sides of the final value theorem for each of the following functions
(i) $2s/(s^2+2s+2)$
(ii) $1/(s^4+4)$ | 7M | 2 | I |
| 3. a) Find the Laplace transform for the following functions
(i) $te^{-2t}u(t)$
(ii) $e^{-2t} \sin 4t u(t)$ | 7M | 2 | I |
| b) Find $f_1(t) \times f_2(t)$
if $f_1(t) = te^{-4t}u(t)$ and $f_2(t) = 5 \cos 3t u(t)$ | 7M | 2 | I |
| 4. a) For the circuit of figure 3, find the value at $t = 0^+$ of (i) V_1 (ii) V_2 | | | |

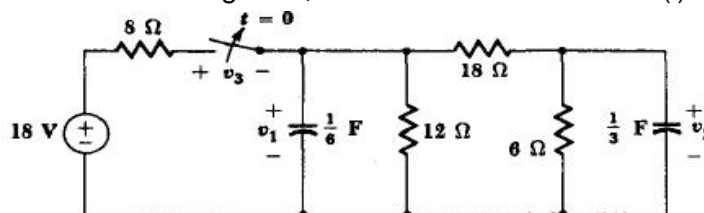


Figure 3

- b) Find
- $i_1(t)$
- ,
- $i_2(t)$
- For the circuit of figure 4,

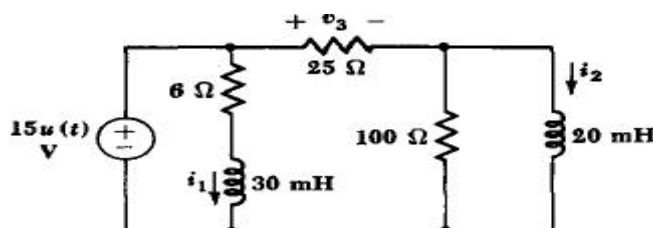


Figure 4

7M 3 I

7M 3 I

5. a) Find $v(t)$ and $i(t)$ if $v(0) = 9\text{ V}$ for the dependent voltage source circuit in figure 5.

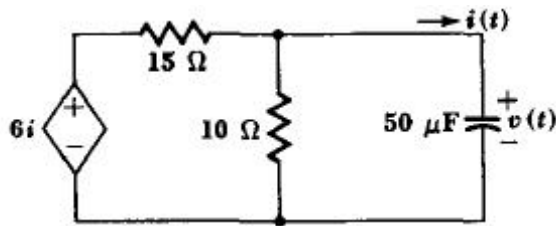


Figure 5

7M 3 I

- b) Find the voltage across each of the three passive circuit elements in figure 6 at $t = 0^+$ if $v_s =$ (i) 0; (ii) 12 V

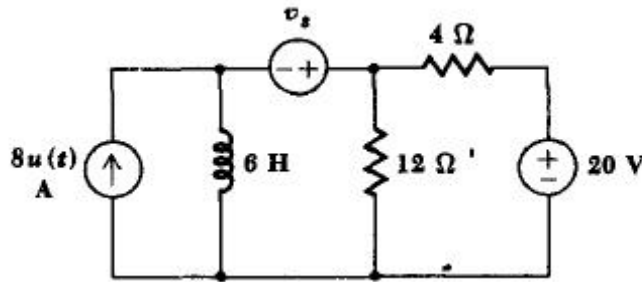


Figure 6

7M 3 I

6. a) Explain the evaluation of Fourier coefficients by symmetry consideration
b) Show that if $f(t)$ is odd, its fourier transform is odd and pure imaginary.
7. a) Explain the elementary the synthesis procedures?

7M 4 II

7M 4 II

7M 5 V

- b) Synthesize $Z(s) = \frac{(s+2)(s+4)}{(s+1)(s+5)}$ into the form shown in figure 7

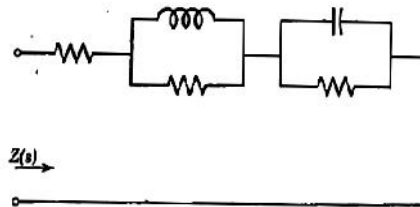


Figure 7

7M 5 II

8. a) Determine the following function is a positive real or not

$$Z(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s}$$

7M 5 V

- b) Synthesize the L-C driving point impedance $Z(s) = \frac{6s^4 + 42s^2 + 48}{s^5 + 18s^3 + 48s}$

In the form shown in figure 8, i.e., determine the element values of the network in henrys and farads

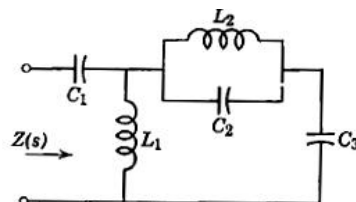


Figure 8

7M 5 V

Hall Ticket Number :

R-17

Code: 7G242

II B.Tech. II Semester Regular & Supplementary Examinations November 2020

Electromagnetic Fields

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five questions from the following (5 x 14 = 70 Marks)

- | | | Marks |
|----|---|-------|
| 1. | a) Find \vec{E} at any point due to a line charge of density λ C/m and length 'L' m. | 7M |
| | b) If $\vec{D} = xy^2(z+1)\vec{a}_x + 20x^2y(z+1)\vec{a}_y + 10x^2y^2\vec{a}_z$ C/m ³ , calculate charge density at $P(0.3, 0.4, 0.5)$. | 7M |
| 2. | a) Derive \vec{B} at $(4, 0, 5)$ from the fundamentals. | 7M |
| | b) On the line $x = 4$ and $y = -4$, there is a uniform charge distribution with density $\rho_L = 25$ nC/m. Determine \vec{E} at $(-2, -1, 4)$ m. | 7M |
| 3. | a) Derive the expression for capacitance of co-axial cable. | 7M |
| | b) A line charge of $20/3$ nC/m is uniformly distributed along a circular ring of radius $r = 2$ m. Find the potential at a point on the axis of a ring 5 m from the plane of the ring. | 7M |
| 4. | a) Using Biot-savart law, find \vec{H} at the centre of a circular conductor. | 7M |
| | b) State and prove Maxwell's third equation. | 7M |
| 5. | a) Using Ampere's circuital law, find \vec{H} due to an infinitely long straight conductor. | 7M |
| | b) A wire is bent into a square coil. Each side of the coil has a length of 20 cm. The coil carries a current of 10 A. The medium is air. Find the vector magnetic potential at the centre of the coil. | 7M |
| 6. | a) Derive an expression for the force between two current carrying conductors in the same direction. | 7M |
| | b) Find self inductance of a solenoid having 500 turns, mean diameter equal to 10 cm and length equal to 5 cm. Assume medium to be air. | 7M |
| 7. | a) Write down Maxwell's equations in their general integral form. | 7M |
| | b) Derive expression for displacement current. | 7M |
| 8. | a) State and explain the Faraday's law of electromagnetic induction | 7M |
| | b) Discuss about motional and transformer induced emf? | 7M |

Code: 7G243

II B.Tech. II Semester Regular & Supplementary Examinations November 2020

Linear Control Systems

(Electrical and Electronics Engineering)


Max. Marks: 70

Time: 3 Hours

Answer any five questions from the following (5 x 14 = 70 Marks)

Marks	CO	Blooms Level
-------	----	--------------

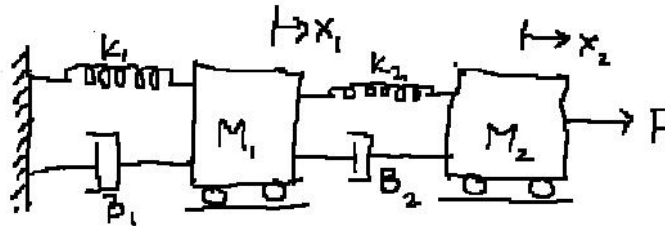1. a) Derive the transfer function relating input F and x_1 for the system shown in figure below



8M

- b) Explain about open loop system and closed loop systems. 6M
2. Derive the expressions for rise time, peak time and maximum peak overshoot of a second order system. 14M
3. a) Explain about different types of test signals. 7M

- b) A unity feedback system is characterized by the open loop transfer function $G(s) = \frac{k}{s(s+10)}$. Determine the gain K , so that the system has a damping ratio of 0.5. For this value of K , determine peak time, settling time, peak overshoot. 7M

4. The open loop transfer function of a control system is given by $G(s)H(s) = \frac{k}{s(s+6)(s^2+4s+13)}$.

Sketch the root locus and determine

- a. The break-away points,
b. The angle of departure
c. The stability condition

14M

5. a) Define stability of a control system and explain about characteristic equation. 4M
- b) The open loop transfer function of a unity feedback system is $G(s) = \frac{K}{(s+2)(s+4)(s^2+6s+25)}$. By applying Routh Criterion, discuss the values of K which will cause sustained oscillations in the closed loop system and the corresponding frequencies 10M

6. The open loop transfer function of a unity feedback system is given by $G(s) = \frac{K(s+20)}{(s+1)(s+2)(s+10)}$. Construct the bode plot for $K = 10$ and determine the phase margin, gain margin, phase crossover frequency and gain cross over frequency. 14M

7. The open loop transfer function of a unity feedback system is $G(s) = \frac{1}{s(1+s)(1+2s)}$. Sketch the polar plot and determine the gain margin and phase margin 14M

8. a) Design the basic lead compensator using Bode plot 7M
- b) Obtain the state space representation of the field controlled DC motor 7M

Hall Ticket Number :									
----------------------	--	--	--	--	--	--	--	--	--

R-17

Code: 7G241

II B.Tech. II Semester Regular & Supplementary Examinations November 2020

AC Machines-I

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five questions from the following (5 x 14 = 70 Marks)

		Marks	CO	Blooms Level
1.	a) Explain the constructional details of Single phase transformers.	7M	1	L2
	b) Explain the losses that occur in Transformers	7M	1	L2
2.	a) Derive the e.m.f equation of Single phase Transformer.	7M	1	L2
	b) Explain the effect of variations of frequency and supply voltage on core losses.	7M	1	L2
3.	a) Explain the principle and operation of an Auto transformer in detail.	7M	2	L2
	b) A single phase transformer working at unity power factor has an efficiency of 90 % at both half load and at the full load of 500 W. Determine the efficiency at 75 % full load.	7M	4	L3
4.	What is meant by 3 – phase transformer groups? What is the significance of these groups? What are the possible connections for a 3 – phase transformer bank? Explain.	14M	3	L4
5.	a) Explain how will you pre determine the efficiency and regulation by conducting OC & SC tests on a single phase transformer with neat circuit diagrams.	7M	2	L2
	b) A 50 kVA, 2200 V/1100 V single phase 50 Hz transformer has a full-load efficiency of 95% and iron loss of 500 W. The transformer is connected as an Auto-transformer to a 3300 V supply. When it delivers a load of 50 kW at unity power factor at 1100 V, Calculate the currents in the windings. Find also the increase in output as auto-transformer also calculate the copper losses as two winding transformer.	7M	4	L3
6.	a) Explain the constructional details of 3 – phase induction motors.	7M	1	L2
	b) A 3 – phase, 50 Hz, 4 – pole induction motor has a slip of 4%. Calculate: (i) Speed of the motor (ii) Frequency of the rotor emf.	7M	4	L4
7.	a) What is circle diagram and what is its significance? How it can be drawn.	7M	1	L2
	b) Explain any one speed control method of 3 – phase induction motor.	7M	3	L2
8.	a) Explain any one starting method of 3 – phase induction motors.	7M	3	L2
	b) Explain the principle of operation of Induction generator.	7M	1	L2
