

Hall Ticket Number :

--	--	--	--	--	--	--	--	--	--

**R-13**

**Code: 1GC41**

II B.Tech. II Semester Supplementary Examinations March 2021

**Mathematics – III**

( Common to EEE & ECE )

Max. Marks: 70

Time: 3 Hours

Answer any **five** questions

All Questions carry equal Marks (**14 Marks** each)

\*\*\*\*\*

1. a) Evaluate  $\int_0^{f/2} \sqrt{\tan u} du$ . 7M  
 b) Prove that  $S(m, 1/2) = 2^{2m-1} S(m, m)$ . 7M
2. If  $w = W + i\mathcal{E}$  represents the complex potential function for an electric field and  $\mathcal{E} = x^2 - y^2 + \frac{x}{x^2 + y^2}$  determine the function  $w$  14M
3. a) If  $\cosh(u+iv) = x+iy$  then prove that  $\frac{x^2}{\cosh^2 u} + \frac{y^2}{\sinh^2 u} = 1$  and  $\frac{x^2}{\cos^2 v} - \frac{y^2}{\sin^2 v} = 1$ . 7M  
 b) Find all the roots of the equation  $\tanh z + 2 = 0$ . 7M
4. Integrate  $f(z) = x^2 + ixy$  from  $A(1,1)$  to  $B(2,8)$  along the curve  $C$  given by  $x = t, y = t^3$  14M
5. a) Find the Taylor's expansion of  $f(z) = \frac{1}{(z+1)^2}$  about the point  $z = -i$ . 7M  
 b) Expand  $f(z) = \frac{1}{(z-1)(z-2)}$  in the regions (i)  $|z| < 1$ , (ii)  $1 < |z| < 2$ . 7M
6. Using Residue Theorem, Evaluate  $\int_{-\infty}^{\infty} \frac{x^2}{(x^2+1)(x^2+4)} dx$  14M
7. a) State and prove Rouché's theorem. 7M  
 b) Prove that the polynomial  $z^5 + z^3 + 2z + 3$  has just one zero in the first quadrant of the complex plane. 7M
8. Find a bilinear transformation which maps the point's  $z = 1, i, -1$  onto the points  $w = 0, 1, \infty$ . 14M

\*\*\*

Hall Ticket Number :										
----------------------	--	--	--	--	--	--	--	--	--	--

<b>R-13</b>
-------------

**Code: 1G343**

II B.Tech. II Semester Supplementary Examinations March 2021

**Pulse and Digital Circuits**

( Electrical and Electronics Engineering )

Max. Marks: 70

Time: 3 Hours

Answer any **five** questions

All Questions carry equal marks (**14 Marks** each)

\*\*\*\*\*

1. a) Determine the upper 3-dB frequency for low pass RC circuit, if a pulse of  $0.5\mu\text{sec}$  is required to pass without distortion. Find the value of resistance if the capacitor is  $0.001\mu\text{F}$ .  
b) List out the applications of attenuator. What is the role of attenuator in CRO probes?
2. a) Write about a positive clamper.  
b) With neat diagram and derivation explain the working of a clipping circuit at two independent levels.
3. Obtain the relation between junction temperature and reverse saturation current and give details.
4. Design a Schmitt trigger circuit to have  $UTP = 6\text{ V}$ ,  $LTP = 3\text{ V}$  using silicon transistors whose  $hFE(\text{min}) = 30$ , and  $IC(\text{on}) = 4\text{mA}$ . Assume necessary data.
5. The specifications of UJT are given as  $\eta = 0.6$ ,  $V_v = 2\text{ V}$ ,  $R_{BB} = 5\text{ k}\Omega$ ,  $I_v = 1.5\text{ mA}$ ,  $I_P = 8\mu\text{A}$  and  $V_{BB} = 18\text{ V}$ . Calculate the component values of the UJT sweep circuit to generate an output sweep frequency of  $10\text{ kHz}$  with sweep amplitude of  $12\text{ V}$ .
6. With the help of the diagram, explain the working principle of a bidirectional diode sampling gate?
7. Draw and explain the block diagram of frequency divider without phase jitter.
8. a) List out the few comparisons of TTL, RTL and CML logic families  
b) Explain the concept of Fan-in and Fan-out.

\*\*\*