

Hall Ticket Number :

R-14

Code: 4G242

II B.Tech. II Semester Supplementary Examinations August 2021

**Electrical Circuits-II**

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)

\*\*\*\*\*

**UNIT-I**

1. a) List out the advantages of three phase system over single phase system. 7M  
 b) Explain the two-wattmeter method of 3- power measurement. 7M

**OR**

2. a) A balanced star connected load has an impedance of  $(8+j6)$  /phase and supply voltage is 415 V, 3- supply. Calculate i) line currents ii) PF iii) Total active power 7M  
 b) Show that  $\tan^{-1} [3 (W_1 - W_2) / (W_1 + W_2)]$  for 3- balanced lagging power factor load. 7M

**UNIT-II**

3. a) State and Prove Initial value theorem and Final value theorem. 7M  
 b) Explain the step response of series RL Circuit using Laplace Transform. 7M

**OR**

4. a) Determine the Laplace transform of the following functions  
 i)  $2\cos^2(t)$  ii)  $t \sin(2t)$  7M  
 b) Calculate initial & final value of the function  $f(t) = 2 + e^{-3t} \cos 2t$  7M

**UNIT-III**

5. a) Explain the significance of initial conditions. 5M  
 b) A series RL circuit with  $R=50$  and  $L=0.2H$  has a Sinusoidal Voltage source  $V(t)=150\sin 500t$ . Determine the expression for  $i(t)$ . 9M

**OR**


6. Derive the expression for current when series RLC Circuit is excited by sinusoidal voltage source  $V(t) = V_m \sin(\omega t + \phi)$  when switch is closed at  $t=0$  14M

**UNIT-IV**

7. a) Explain all wave form symmetry by using relevant examples. 7M  
 b) Discuss properties of Fourier transforms. 7M

**OR**

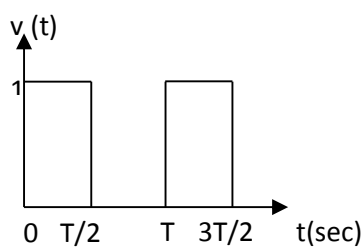8. a) Illustrate the trigonometric Fourier series expansion of the waveform shown in fig



- b) Determine Fourier transform of Gaussian function. 7M

**UNIT-V**

9. a) Explain the necessary conditions for a transfer function 7M  
 b) Synthesize the given impedance function using elementary synthesis.

$$Z(s) = \frac{6s^3 + 3s^2 + 6s + 2}{3s^3 + 3s}$$

**OR**

10. Determine the Cauer form I and II realizations for  $Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$  14M

\*\*\*

Hall Ticket Number :

R-14

Code: 4G244

II B.Tech. II Semester Supplementary Examinations August 2021

**Linear Control Systems**

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)


\*\*\*\*\*

**UNIT-I**

1. a) Define control system. State the difference between closed loop and open control system with examples 7M
- b) Define transfer function. Find the transfer function of closed loop control system 7M

**OR**

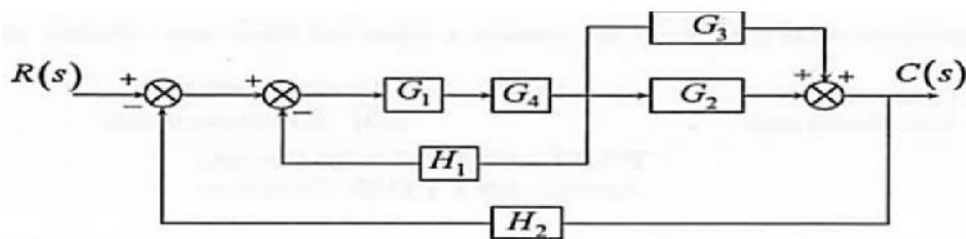2. a) Determine the closed loop transfer function of the given system using block reduction technique.



- b) Describe the block diagram reduction rules with figures.

**UNIT-II**

3. Derive the time domain specifications of a second order system 14M

**OR**

4. a) Derive the response first order system with unit ramp input 7M
- b) Determine the step, ramp and parabolic error constant of unity feedback control system whose forward path transfer function is given as  $G(s) = \frac{K(1+2S)(1+4S)}{S^2(S^2+S+1)}$ . Also determine steady state error. 7M

**UNIT-III**

5. a) Define stability, asymptotic stability and relative stability. 7M
- b) What are the difficulties in forming Routh array? Explain how to overcome. 7M

**OR**

6. The characteristic polynomial of a system is  $s^7+9s^6+24s^5+24s^4+24s^3+24s^2+23s+15=0$ . Determine the location of the roots in s-plane and hence stability of the system. 14M

**UNIT-IV**

7. a) Derive the frequency domain specifications of a second order system 10M
- b) List the advantages and disadvantages of Frequency response 4M

**OR**

8. a) Define GM & PM. 4M
- b) Explain the procedure to determine the Gain margin and Phase margin from Polar plot. 10M

**UNIT-V**

9. a) Derive the expression for the transfer function of a lag-lead compensator. 6M
- b) Define lag compensator and draw the Pole Zero Plot. Also state its effects. 8M

**OR**

10. The open-loop transfer function of a unity feedback control system is given by  $G(s)H(s) = \frac{K}{S(1+0.2S)}$ . Design a suitable compensator such that the system will have  $K_v=2$  and  $PM = 50^\circ$  14M

\*\*\*

Code: 4GC41

II B.Tech. II Semester Supplementary Examinations August 2021

**Mathematics-III**

( Common to EEE &amp; ECE )

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit ( 5x14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

1. a) Symmetry of Beta function  $B(m, n)=B(n, m)$  7M

- b) Evaluate  $\int_0^1 \frac{x^2}{\sqrt{1-x^5}} dx$  in terms of B function 7M

**OR**

2. a) Find real and imaginary parts  $\cot z$  7M

- b) Find all the roots of  $\sin z = 2$  7M

**UNIT-II**

3. Determine P such that the function  $f(z) = \frac{1}{2} \log(x^2 + y^2) + i \tan^{-1} \left( \frac{px}{y} \right)$  be an analytic function 14M

**OR**

4. Find an analytic function whose real part is  $e^{-x} [x \sin y - y \cos y]$  14M

**UNIT-III**

5. Evaluate  $\int_c (y^2 + 2xy) dx + (x^2 - 2xy) dy$  where  $c$  is the boundary of the region by  $y = x^2$  and  $x = y^2$  14M

**OR**

6. Expand  $\log z$  by Taylor's series about  $z=1$ . 14M

**UNIT-IV**

7. a) Find the poles and Residues at each pole  $\frac{ze^z}{(z-1)^3}$  7M

- b) Use Residue theorem to find the number of zeros of the polynomial  $z^{10} - 6z^7 + 3z^3 + 1$  if  $|z| < 1$  7M

**OR**

8. Evaluate  $\int_c \frac{e^{2z}}{(z-1)(z-2)} dz$  where  $c$  is the circle  $|z| = 3$  14M

**UNIT-V**

9. Find the bilinear Transformation which maps the point  $(-1, 0, 1)$  into the points  $(0, i, 3i)$ . 14M

**OR**

10. Find the image of the region in the  $z$ -plane between the lines  $y=0$  and  $y = \frac{f}{2}$  under the Transformation  $w = e^z$ . 14M

\*\*\*

Hall Ticket Number :

**R-14**

**Code: 4G346**

II B.Tech. II Semester Supplementary Examinations August 2021

**Pulse and Digital Circuits**

( Electrical and Electronics Engineering )

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit ( 5x14 = 70 Marks )

\*\*\*\*\*

**UNIT-I**

1. a) Discuss the application of Attenuator as a CRO probe 8M  
b) Define the following:  
i) Linear wave Shaping ii) Lower cutoff frequency iii) Rise time 6M
- OR**
2. A 10 Hz square wave is fed to an amplifier. Calculate and plot the output waveform under the following conditions. The lower 3-dB frequency is a) 0.3 Hz b) 3 Hz c) 30Hz 14M

**UNIT-II**

3. a) State and Prove the clamping circuit theorem. 8M  
b) Explain the operation of a two level diode clipper with the help of circuit diagram? 6M
- OR**
4. a) Explain the diode switching times with their neat diagrams 10M  
b) Explain piecewise linear characteristics of the diode 4M

**UNIT-III**

5. Draw the circuit diagram of Fixed Bias Bistable Multivibrator and explain its operation with the help of wave forms at base and collector 14M
- OR**
6. Find the Lower and Upper Threshold voltage for Schmitt trigger circuits with following data. Assume transistors with  $h_{fe}=30$ ,  $V_{cc}=12V$ ,  $R_{c1}=4K$ ,  $R_{c2}=1K$ ,  $R_1=2K$ ,  $R_s=1K$ ,  $R_2=6K$ ,  $R_e=3K$  14M

**UNIT-IV**

7. a) How is linearity corrected through adjustment of the driving waveform for a Current Time Base Generator 8M  
b) What are the applications of Time Base Generators 6M
- OR**
8. a) Illustrate the working principle of Bootstrap time base generator 7M  
b) Explain transistor Miller time base generator with neat diagram 7M

**UNIT-V**

9. a) Explain about unidirectional sampling gate with neat sketch 8M  
b) Discuss the advantages and disadvantages of Unidirectional sampling gate 6M
- OR**
10. a) Verify the truth table of CMOS NOR gate with neat sketches 10M  
b) What are the applications of sampling gates? 4M

\*\*\*