

Code: 7GC43

II B.Tech. II Semester Supplementary Examinations November 2023

Complex Variables & Special Functions

(Common to EEE & ECE)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)

UNIT-I

1. a) Symmetry of Beta function $B(m, n) = B(n, m)$ 7M

- b) Evaluate $\int_0^1 \frac{x^2}{\sqrt{1-x^5}} dx$ in terms of B function 7M

OR

2. Prove that $\int_0^{\frac{\pi}{2}} \sin^2 x \cos^4 x dx = \frac{\pi}{32}$ 14M

UNIT-II

3. Determine P such that the function $f(z) = \frac{1}{2} \log(x^2 + y^2) + i \tan^{-1}\left(\frac{px}{y}\right)$ be an analytic function 14M

OR

4. Prove that z^n (n is a positive integer) is analytic and hence find its derivative. 14M

UNIT-III

5. Expand $\log z$ by Taylor's series about $z=1$. 14M

OR

6. Evaluate $\int_{(0,0)}^{(1,1)} (3x + 4xy + ix^2) dz$ along $y = x^2$ 14M

UNIT-IV

7. Find the poles of the function $\frac{z+1}{z^2(z-2)}$ and Residues at the poles 14M

OR

8. Evaluate $\oint_c \frac{4-3z}{z(z-1)(z-2)} dz$ where c is the circle $|z| = \frac{3}{2}$ using Residue theorem. 14M

UNIT-V

9. Under the Transformation $w = \frac{1}{z}$ find the image of the circle $|z-2i| = 2$ 14M

OR

10. Show that the function $w = \frac{4}{z}$ transforms the straight line $x=c$ in the z-plane into a circle in the w-plane. 14M

Code: 7G244

II B.Tech. II Semester Supplementary Examinations November 2023

Electrical Circuits – II

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)

UNIT-I

1. a) Prove $I_L = 3 I_{ph}$ for 3- , balanced, - connected system. 7M
- b) Illustrate the readings of two wattmeter's on a 3-wire, 240V system with balanced star connected load of $10\angle 30^\circ$. 7M

OR

2. a) A three phase balanced system supplies 230V to a delta connected load whose phase impedances are equal to $(3.54+j3.54)$. Determine the line current and draw the phasor diagram 7M
- b) An induction motor draws a three phase power. Two wattmeter measurement is applied to find total power. If $W_1 = 10KW$ and $W_2 = 5KW$ determine the total active power, reactive power and power factor. 7M

UNIT-II

3. a) State and Prove Initial value theorem and Final value theorem. 7M
- b) Determine the Laplace transform of the following functions
i) $f(t) = (4t^3 + t^2 - 6t + 7)$ ii) $e^{-4t}\sin 5t$ 7M

OR

4. Formulate the step response of series RLC Circuit using Laplace Transform. 14M

UNIT-III

5. Derive the expression for current response of RL series circuit with a DC excitation. 14M
- OR**
6. Derive the expression for current response of RC series circuit with a sinusoidal excitation. 14M

UNIT-IV

7. a) Discuss properties of Fourier transforms. 7M
- b) Explain the evaluation of trigonometric Fourier coefficients 7M
- OR**
8. a) Determine Fourier transform of Gaussian function. 7M
- b) Determine the exponential Fourier series for the half wave rectifier sine wave 7M

UNIT-V

9. a) Test the function $H(s) = 4s^6 + 2s^5 + 17s^4 + 8s^3 + 16s^2 + 6s + 3$ is Hurwitz or not 7M
- b) Explain the necessary conditions for a transfer function 7M
- OR**
10. Test the positive realness of the following function

$$F(s) = \frac{(s^2 + 2s + 36)}{(s^2 + 3s + 49)}$$

14M

Hall Ticket Number :

R-17

Code: 7G345

II B.Tech. II Semester Supplementary Examinations November 2023

Analog Electronics-II

(Electrical and Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)

UNIT-I

1. a) With a neat circuit diagram explain basic operational amplifier circuit 6M
- b) Describe the internal block diagram of an Op-amp and explain each block in detail 8M

OR

2. a) Derive the gain of non inverting amplifier 7M
- b) Design an non inverting Op Amp with gain 120. 7M

UNIT-II

3. a) Illustrate the operation of inverting summer circuit using IC 741. 7M
- b) Illustrate the operation of Subtractor circuit using IC 741. 7M

OR

4. a) Discuss the operation of Adder-Subtractor using Op-Amp. 7M
- b) Consider the lossy integrator with components $R_1=10\text{ K}$, $R_F=100\text{ K}$, $C_F=10\text{nF}$. Determine the lower frequency limit of integrator. 7M

UNIT-III

5. a) Explain the operation of Precision Half-wave Rectifier. 7M
- b) Discuss the operation of Log Amplifier. 7M

OR

6. a) Design a triangular wave generator using comparator and integrator to oscillate at 4KHz and peak to peak voltage of 7V. Use the Op-Amp with $\pm 15\text{V}$ power supply and make necessary assumptions. 6M
- b) Explain how astable multivibrator can be used as Square wave generator. 8M

UNIT-IV

7. a) Draw the pin diagram of IC 555 and list out its applications 6M
- b) Explain the basic principle of operation using block schematic of a PLL. 8M

OR

8. a) Discuss how PLL can be used as frequency translator. 7M
- b) How a monostable multivibrator can be used as missing pulse detector? Explain. 7M

UNIT-V

9. a) With help of neat diagram explain the operation of counter type ADC. 7M
- b) Illustrate the operation of weighted resistor DAC. 7M

OR

10. a) What are the advantages of SAR ADC? Explain its operation 7M
- b) Construct the Inverted R-2R DAC and explain in detail 7M
