	Н	all Ticket Number :													
Į	Co	de: 1G354		<u> </u>										R-11 / R-13	
	III B.Tech. I Semester Supplementary Examinations May 2017														
	Antennas and Wave propagation														
	(Electronics & Communication Engineering)														
	Max. Marks: 70 Time: 3 Hours														
	Answer any five questions All Questions carry equal marks (14 Marks each) ********														
1.	1. a) Deduce the relationship between Gain and Directivity of an antenna?													7M	
	b) An antenna has normalized radiation intensity														
	$U(_{''}, W) = \begin{cases} 10 \sin_{''} \sin W, W / sr & 0 <_{''} < f, 0 < W < f \\ 0 & else where \end{cases}$														
	0 else where														
	Find the power radiated and directivity.											7M			
2.	a) Sketch the patterns of a centre fed vertical diploes of the following lengths?											ths?			
		i) $\frac{3}{2}$ ii) $\frac{33}{2}$													
	$\frac{1}{2}$ $\frac{1}{2}$ $\frac{1}{2}$												6M		
	b)	Starting from Maxw		•				•					•		4M
	c)	c) A transmitting antenna has an effective height of 61.4 mts and takes rms current of													
	50 Amps at a wavelength of 625 mts. Find radiation resistance, radiated power an Antenna efficiency if the antenna loss resistance is 5 .													nated power and	4M
3	a)	-									catior	י.			6M
0.	b)	With an example explain the principle of pattern multiplication? Obtain an array factor for a rectangular array of isotropic radiators which are excited in											0.01		
	/	phase and are p				-		-							
		wavelength?													8M
4.	a)	Explain the operat	ion o	f Hel	ical a	anter	na ir	n axia	al mo	de?					7M
	b)	Calculate the dian produce a beam-wi					•				•			lector required to	7M
5.	a)	Explain the metho	d of r	neas	uring	g the	Bear	m wie	dth o	fana	anter	nna?			7M
	b)												7M		
6.	a)	Explain the following	•						_						
	LA	i) Earth's beh					•			,	Wav			had a south as	6M
	b)	A vertically polariz wave along a smo The frequency of t	oth g	grour	nd ha	iving	diele	ectric	cons	stant	20 a	and c	onduc	ctivity 2X10 ⁻² /m.	OM
7	a)	the ground. Derive an express	ion fr	or rad	tio ha	orizo	n die	tance	for	curv	ad as	orth?			8M 7M
1.	a) b)	Explain the following				51120	11 115	ance		Curve	eu ea	ai (11) (7 111
	5)	i) Tropospheric Scatter Propagation ii) Super Refraction											7M		
8.	a)	Explain how the e ionosphere?	earth	's m	agne	tic fi	eld e	effect	s the	e pro	paga	ation	of ra	dio waves in the	6M
	 b) A wave propagating through ionosphere at a height of 400km above the earth surface at a frequency of 10MHz, Determine the skip distance for both flat and curved earth, assume the refractive index of the medium is 0.9 										8M				

Hall T	icket Number :]
Code: 1	G457 R-11 / R	-13
	III B.Tech. I Semester Supplementary Examinations May 2017	
	Computer Systems Architecture	
Max. M	(Electronics and Communication Engineering) arks: 70 Time: 3 H	lours
	Answer any <i>five</i> questions	10010
	All Questions carry equal marks (14 Marks each)	
1. a)	Convert the following octal numbers into binary and hexadecimal:	
	(i) $5436.15_8 = ?_2 = ?_{16}$ (ii) $13705.207_8 = ?_2 = ?_{16}$	10M
b)	List different types of computers and write significance of each type	4M
2. a)	Write about register transfers and Register Transfer language with an example	8M
b)	Explain Arithmetic Micro Operations, logic micro operations,	6M
3.	With a neat diagram explain the BUS organization for seven CPU registers	14M
4. a)	Discuss the design of control unit.	7M
b)	Explain about address sequencing in Micro Programmed control Unit with an example	7M
5. a)	Compute square root for 172_{10} using binary square root algorithm.	8M
b)	Develop a flow chart for the Booth's multiplication algorithm.	6M
6. a)	Explain various cache memory management techniques	8M
b)	Write about associate Memory	6M
7. a)	Discuss in detail about Direct Memory Access (DMA)	8M
b)	write about peripheral Component interconnect (PCI) bus	6M
8. a)	Explain Arithmetic Pipelining processing with an example	8M
b)	Distinguish between parallel processing and pipelining processing	6M
,	***	

Hall Ticket Number :]								
Code: 1G353	-13								
III B.Tech. I Semester Supplementary Examinations May 2017									
Digital IC Applications (Electronics & Communication Engineering)									
Max. Marks: 70 Time: 3 H	lours								
Answer any Five questions All Questions carry equal marks (14 Marks each) *********									
 a) Explain the operation of a three input NOR gate and Design a CMOS transisto circuit for the same? 	or 7M								
 b) Does speed and the power consumption of a CMOS device depend on it dynamic electrical characteristics? Justify. 	s 7M								
2. a) Explain the classification of TTL logic family and mention its two applications.									
b) Compare the logic families Emitter coupled logic and CMOS logic in detail.	6M								
3. a) Explain the various Data types and Operators used in VHDL.	7M								
 b) State the built-in libraries and packages in VHDL. Explain about the use defined packages in VHDL. 	er 7M								
 a) Write the VHDL entity and architecture for an eight bit inverter in structura model using FOR-GENERATE loop. 	al 7M								
 b) What is Time dimension? Write a VHDL code for generating input waveforms i a test bench using WAIT statement. 	n 7M								
5. a) Explain 74x138 like 3 to 8 decoder and develop the VHDL code for it in Dataflow model.	n 7M								
b) Discuss about EXOR gates and parity circuits in detail?	7M								
 a) What is a barrel shifter? Design an approach to build a 16-bit barrel shifte using 74x151 ICs. 	er 6M								
b) What is Ones counter? Draw the architecture for a 32 bit ones counter and write the VHDL code for it?	d 8M								
7. a) Draw the positive edge triggered D-Flip Flop with preset and clear using gates And explain its operation?	s. 6M								
b) What do you mean by modulo-m-counter? Explain about Ripple and Synchronous counters in detail?	d 8M								
8. a) Draw the internal structure of synchronous SRAM and explain its operation in detail.	n 8M								
 b) What is 2D-decoding? Write briefly about commercial ROMs. *** 	6M								

Hall Ti	icket Number :]									
Code:	1G352 R-11 / R-	13									
	III B.Tech. I Semester Supplementary Examinations May 2017										
	Linear IC Applications										
Max. N	(Electronics & Communication Engineering) Aarks: 70 Time: 3 Ho Answer any five questions	ours									
	All Questions carry equal marks (14 Marks each)										
1. a)	What is the purpose of Differential amplifier and explain the low frequency small signal analysis of it.										
b)	Explain the difference between constant current bias and current mirror.	7M									
2. a)	Draw the schematic symbol and block diagram of the typical op-amp and explain.										
b)	Define the following terms as applied to op-amp and mention their typical values for IC741.										
	i)CMRR ii) Slew rate iii) PSRR iv)Input offset voltage	8M									
3 a)	Explain the difference between integrator and differentiator and give one application of each.										
b)	Draw and explain the operation of a current to voltage converter. If 741C is used, what is the lowest value of current that may be measured?	7M									
4. a)	List the important characteristics of the comparator and explain some applications of it.	7M									
b)	Draw the circuit diagram of log and antilog amplifiers and derive their output voltages.	7M									
5. a)	Design a second-order low pass Butterworth filter at a cutoff frequency of 1KHz. Draw the frequency response of the same filter using $A_F=1.586$	10M									
b)	What is an all pass filter? Where and why is it needed?	4M									
6. a)	Explain the Astable operation of 555 timer and derive the expression for its frequency and duty cycle.	8M									
b)	Explain the block diagram of PLL emphasizing the capture range and lock range.	6M									
7. a)	Describe the operation of dual slope A/D converter with necessary diagrams. Give some of its advantages & disadvantages.	7M									
b)	How many resistors are required for an 8 bit weighted resistors D/A converter? What are those resistor values , assuming the smallest resistance is R.	7M									
8. a)	What is the difference between analog multiplier and modulator? Explain the balanced modulator in detail.	7M									
b)	Draw a sample and hold circuit. Explain its operation and indicate its uses.	7M									

Hall Ticket Number :]			
Code: 1GA51							R	-11 / R-13	3						
Coue.		Sem	este	r Si	Inn	lem	enta	nrv I	- - Xar	nina	ntio	ns M	av	2017	
III B.Tech. I Semester Supplementary Examinations May 2017 Managerial Economics and Financial Analysis															
(Common to CE, ME and ECE)															
Max.	Marks: 70												-	Time: 3 Hou	irs
Answer any Five questions All Questions carry equal marks (14 Marks each)															
1.	1. What is Managerial Economics? Discuss its relation with other areas of Management?														
2.	Explain various Demand forecasting techniques with suitable examples?														
3.	Define Production function? Explain about Cobb-Douglas production function?														
4.	How do you monopoly ma		•	ma	rket	s? E	Discu	ss p	orice	out	put	dete	rmir	nation in	
5.	What is the n public sector							ess (orgar	nizat	ions	? Exp	olair	n various	
6.	What is Capit	al bu	ıdget	ing?	Disc	cuss	vario	ous r	nethe	ods (of ca	pital	bud	geting?	
7.	What is Tra accounting?	il ba	alanc	ce?	Expl	ain	its I	role	and	imp	oorta	ince	in	financial	
8.	What is Rat analysis?	io A	Analy	sis?	Dis		s va **	rious	s fina	ancia	al ra	atios	in	financial	