

Hall Ticket Number :									
----------------------	--	--	--	--	--	--	--	--	--

**R-17**

**Code: 7G352**

III B.Tech. I Semester Supplementary Examinations June 2022

**Control Systems**

(Electronics and Communication Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)

\*\*\*\*\*


Marks

**UNIT-I**

- 1. a) List out the advantages and drawbacks of open loop and closed loop control systems 7M
- b) Explain the feedback characteristics of closed loop control system 7M

**OR**

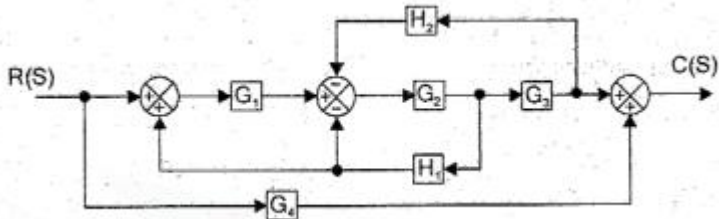- 2. a) Determine the closed loop transfer function  $C(s)/R(s)$  of the system as shown figurer below 10M



- b) Classify the types of control systems 4M

**UNIT-II**

- 3. a) Discuss about procedural steps to sketch root locus 7M
- b) Find the breakaway point and angle of departure of a unity feedback system has open loop transfer function  $G(s) = K/s(s^2+4s+13)$  7M

**OR**

- 4. Obtain the steady state error  $e_{ss}$  of Type-0, Type-1 and Type-2 systems for unit step, ramp and parabolic inputs 14M

**UNIT-III**

- 5. a) Explain about frequency domain specifications 7M
- b) Describe the procedure for developing the polar plot 7M

**OR**

- 6. Define the following terms 14M
  - (i) Gain cross over frequency   (ii) Phase cross over frequency
  - (iii) Gain margin                   (iv) Phase margin

**UNIT-IV**

- 7. a) Discuss about controllers. Explain about different types of controllers 7M
- b) Discuss the design procedure of PID controller 7M

**OR**

- 8. a) Distinguish the lead and lag compensators 7M
- b) Calculate the transfer function of lead compensator 7M

**UNIT-V**

- 9. a) Discuss the significance of state space analysis 7M
- b) Define the terms controllability and observability and write necessary conditions for verification of controllability and observability 7M

**OR**

- 10. Define (i) state   (ii) state variables   (iii) state space representation 14M

\*\*\*

Hall Ticket Number : 

--	--	--	--	--	--	--	--	--	--	--

**R-17**

**Code: 7G353**

III B.Tech. I Semester Supplementary Examinations June 2022

**Analog & Digital Integrated Circuits Applications**

(Electronics and Communication Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five full questions by choosing one question from each unit (5x14 = 70 Marks)

\*\*\*\*\*

Marks

**UNIT-I**

1. Discuss the operation of Op-Amp block diagram and its characteristics 14M

**OR**

2. a) Identify the applications of Op-amp and its advantages. 7M

b) List out the characteristics of Ideal Op-amp. 7M

**UNIT-II**

3. a) Explain the functional diagram of IC 555 with a neat sketches 8M

b) List out the applications of PLL 6M

**OR**

4. a) Restate the operation of Zero Cross Detector and Window Detector 7M

b) Analyze the basic principle of successive approximation type ADC 7M

**UNIT-III**

5. a) Design 2-input NOR gate using CMOS Logic. 7M

b) Differentiate between CMOS and TTL families. 7M

**OR**

6. Summarize the steady state electrical behavior of CMOS circuits 14M

**UNIT-IV**

7. a) Design Full adder using half adders. 8M

b) Discuss about logic gates used Combinational Circuits 6M

**OR**

8. Define decoder and explain with neat diagram the functionality of 3 to 8 decoder also write the VHDL program for standard 74X138. 14M

**UNIT-V**

9. a) Differentiate between latches and Flip-Flops. 7M

b) Evaluate the Characteristic equations of SR and JK Flip-Flops. 7M

**OR**

10. Design 3-bit SISO Shift register using Flip-Flops. 14M

\*\*\*