

--	--	--	--	--	--	--	--	--	--

Code: 1G281

IV B.Tech. II Semester Regular & Supplementary Examinations September 2020

Power Semiconductor Drives

(Electrical & Electronics Engineering)

Max. Marks: 70

Time: 3 Hours

Answer any five questions

All Questions carry equal marks (14 Marks each)

1. a) Explain speed-torque characteristics of a 1- fully controlled converter connected to separately excited D.C motor with continuous current operation. Draw the relevant wave forms. 7M
- b) Explain the operation of single phase semi-converter fed separately excited D.C. series motor drive with necessary diagrams. 7M
2. a) Derive the output voltage expression and Speed Torque characteristics for a three phase fully controlled rectifier fed DC separately excited motor with neat circuit diagram and wave forms 10M
- b) Discuss the reason for the neglecting of discontinuous conduction in three phase rectifier fed motors? 4M
3. a) Define Braking? And give brief discussion on various types of braking. 4M
- b) A 220V, 1000rpm, 60A separately excited motor with armature resistance of 0.6Ω fed from a Circulating current dual converter with AC source voltage line voltage=165V. Determine converter firing angles for the following operating points:
 - i. Motoring operation at rated motor torque and 900rpm
 - ii. Braking operation at rated motor torque at 900 rpm
 - iii. Motoring operation at rated motor torque and -900 rpm
 - iv. Braking operation at rated motor torque at -900 rpm 10M
- 4 a) Discuss with the suitable diagrams I quadrant and II quadrant choppers. 7M
- b) A 220 V, 24 A, 1000 rpm separately excited dc motor having an armature resistance of 2Ω is controlled by a chopper. The chopping frequency is 500 Hz and the input voltage is 230 V. Calculate the duty ratio for a motor torque of 1.2 times rated torque at 500rpm 7M
5. a) Explain with relevant equations and circuit diagrams of equivalent circuit of a Induction Motor ? 4M
- b) Explain with neat circuit diagram about single phase & three phase AC Voltage controller fed Induction motor 10M
6. a) Brief the concept of v/f control for the speed control of Induction motor 7M
- b) Discuss in detail about the Variable Frequency control from Voltage Source with v-f relation ,speed – torque characteristics and relevant equations 7M
7. a) What is slip power recovery scheme? Explain with relevant diagrams. 7M
- b) Discuss the static Scherbius drive with relevant diagrams 7M
8. Describe the open-loop and closed loop methods of speed control of a synchronous motor using VSI 14M
