

--	--	--	--	--	--	--	--	--	--

**Code: 4PC314***M.Tech. I Semester Regular & Supplementary Examinations Feb/Mar 2016***Modelling & Synthesis through Verilog HDL***(Common to DECS & VLSISD)*

Max. Marks: 60

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 12 = 60 Marks )

\*\*\*\*\*

**UNIT-I**

1. Explain about various Data types available in Verilog 12M

**OR**

2. Explain about various Operators available in Verilog. 12M

**UNIT-II**

3. Explain about Models of Propagation Delays in Verilog. 12M

**OR**

4. Explain about Inertial Delay and Transport Delay in Verilog. 12M

**UNIT-III**

5. Explain about Procedural Timing Control and Synchronization. 12M

**OR**

6. Explain about Constructs for Activity Flow Control in Verilog. 12M

**UNIT-IV**

7. Explain about HDL-based Synthesis of Combinational Logic in Verilog. 12M

**OR**

8. Explain about Synthesis of Finite State Machine (FSM) in Verilog. 12M

**UNIT-V**

9. Explain about Synthesis of Expressions and Operators for language constructs. 12M

**OR**

10. Explain about Synthesis of Assignments for language constructs 12M

\*\*\*

**Code: 4PC311***M.Tech. I Semester Regular & Supplementary Examinations Feb/Mar 2016***VLSI Technology***(Common to Embedded Systems & VLSISD)*

Max. Marks: 60

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 12 = 60 Marks )

\*\*\*\*\*

**UNIT-I**

1. a) Derive the  $I_{DS}$  versus  $V_{DS}$  expression of a NMOS transistor. 6M  
 b) Draw the simple BICMOS inverter and explain its operation. Mention its drawbacks and give suitable remedies. 6M

**OR**

2. a) Explain the design of CMOS inverters with neat expressions. 6M  
 b) Explain the parameters  $G_m$ ,  $G_{DS}$ ,  $W_O$  with respect to a MOS device. 6M

**UNIT-II**

3. a) Explain the concept of wires. 3M  
 b) Explain the scalable design rules in detail with neat diagrams. 9M

**OR**

4. a) Discuss the transistor structures in detail. 6M  
 b) Explain the concept of layout design tools. 6M

**UNIT-III**

5. a) Explain the advantages and drawbacks of Static complementary gates. 6M  
 b) Explain the concept of resistive interconnect delays. 6M

**OR**

6. a) Discuss the alternate gate circuits with neat diagrams. 6M  
 b) Design a 3 input NOR gate and explain its operation. 6M

**UNIT-IV**

7. a) Explain the concept of Interconnect design. 6M  
 b) Discuss the switch logic networks in detail. 6M

**OR**

8. a) Write a short note on simulation. 6M  
 b) Draw the layout of a 3 input NAND gate. 6M

**UNIT-V**

9. a) Discuss the concept of Off chip connections. 6M  
 b) Give the concept of Power optimization. 6M

**OR**

10. a) Explain the concept of High level synthesis in detail. 6M  
 b) Discuss the concept of Clocking disciplines. 6M

\*\*\*

**Code: 4PC312***M.Tech. I Semester Regular & Supplementary Examinations Feb/Mar 2016***Analog IC Design**  
(VLSI System Design)

Max. Marks: 60

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 12 = 60 Marks )

\*\*\*\*\*

**UNIT-I**

1. a) Explain in detail about large signal and small signal modeling of BJT
- b) Discuss the operation of common gate amplifier circuit with current mirror as active load

**OR**

2. a) Explain why source/emitter follower circuits exhibits large amounts of overshoot and ringing
- b) Derive the necessary equations to evaluate the output impedance of an emitter follower Bipolar gain stage with a help of a circuit diagram

**UNIT-II**

3. a) What are the ways of improving slew rate of 2-stage CMOS OPAMP? And derive an expression for slew rate of CMOS OPAMP.
- b) Explain about various OPAMP compensation techniques

**OR**

4. a) What is CMFB circuit? What are various methods of designing CMFB circuits? And compare them.
- b) Explain the principle of continuous time CMFB circuit

**UNIT-III**

5. a) Explain the correlated double sampling techniques with suitable example.
- b) Draw the circuit of switched capacitor circuit and explain its principle

**OR**

6. Write short note on
  - a. First order filter
  - b. Biquard filters

**UNIT-IV**

7. Write short note on
  - a. Hybrid Converters
  - b. Nyquist rate Converters

**OR**

8. a) Explain the characteristic parameters of A/D and D/A converters in detail
- b) Explain the role of Quantizing error in the Process of conversion

**UNIT-V**

9. a) Explain about the Digital decimation filters
- b) Derive the component values of 1<sup>st</sup> order continuous time filter.

**OR**

10. a) What are the practical considerations of over sampling converters
- b) Explain about the band pass over sampling Converters

\*\*\*

**Code: 4PC313***M.Tech. I Semester Regular & Supplementary Examinations Feb/Mar 2016***Digital IC Design**

(Common to Embedded Systems &amp; VLSI System Design)

Max. Marks: 60

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 12 = 60 Marks )

\*\*\*\*\*

**UNIT-I**

1. Design Static CMOS inverter and analyze its behavior using switch models. 12M

**OR**

2. a) Describe significant advantages of dynamic logic over static logic. 6M  
b) What are all the effects of supply voltage scaling in CMOS inverter? Explain in brief. 6M

**UNIT-II**

3. a) What are the advantages of NORA logic? Also explain the need of NORA logic. 6M  
b) Design a full adder using Domino logic gates. 6M

**OR**

4. Design 3 to 8 decoder in NORA logic. Use 2 to 4 decoder while implementing 3 to 8 decoder. 12M

**UNIT-III**

5. a) Explain the adiabatic approach to CMOS VLSI design technique. 6M  
b) Derive the expression for short circuit power consumption in CMOS circuits and relate drain current ( $I_D$ ), drain voltage ( $V_{DD}$ ). 6M

**OR**

6. a) Define guard evolution. Explain its role in switching activity of CMOS XOR logic circuit. 6M  
b) Explain how bus multiplexing effects on logic effort in CMOS NAND gate. Find its logic effort value. 6M

**UNIT-IV**

7. a) What are the precautions to be taken during global routing and mention its layout lambda based design limitations for CMOS. 6M  
b) Calculate the equivalent sheet resistance for two NMOS inverters connected in cascaded. Assume  $\left(\frac{W}{L}\right)_p = 60$ ,  $\left(\frac{W}{L}\right)_n = 40$ , Sheet resistance as  $R_s$ , Delay time as . 6M

**OR**

8. a) Explain the function to drive large capacitance load ( $C_{LOAD}$ ) in low power CMOS circuits. Find the resonance frequency  $f_{RES}$  in terms of  $R_{LOAD}$  and  $C_{LOAD}$ . 6M  
b) Describe full custom layout design for CMOS circuit. 6M

**UNIT-V**

9. a) Write the design procedure for Modified Booth Multiplier. 6M  
b) Give the transistor level realization of Adder/ Subtractor. 6M

**OR**

10. a) What are the design criteria reviewed in CMOS static RAM cell design? 6M  
b) Explain how ALU functions implemented using adders and multipliers. 6M

\*\*\*

**Code: 4PC315***M.Tech. I Semester Regular & Supplementary Examinations Feb/Mar 2016***FPGA Architectures and Applications***(Common to Embedded Systems & VLSISD)*

Max. Marks: 60

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 12 = 60 Marks )

\*\*\*\*\*

**UNIT-I**

1. a) Distinguish between Altera's MAX 5000 and MAX7000 series PLDS. 6M  
 b) Explain Cypress Flash 370 Device Technology. 6M

**OR**

2. a) With a neat sketch of MAX 5000 device macro cell. Explain how the sequential logic is implemented. 6M  
 b) Implement the following Boolean function using a suitable PAL  
 $F(a, b, c, d) = m(2,4,6,8,10,11,12,14,15)$ . 6M

**UNIT-II**

3. a) Draw and explain logic blocks of FPGAs. 6M  
 b) List the Actel based FPGAs and give their speed performance. 6M

**OR**

4. a) Distinguish between FPGA Design Flow and ASIC Design Flow. Explain FPGA Routing Architecture with all the steps. 6M  
 b) Explain the Technology mapping for FPGAs. 6M

**UNIT-III**

5. a) Give brief comparison of Act1, Act2 and Act3 FPGAs. 6M  
 b) What are the salient features of Altera's FLEX 8000 FPGA logic element? 6M

**OR**

6. a) Explain the AT & T-ORACs (Optimized Reconfigurable Cell Array). 6M  
 b) Speed performance in system programmability. 6M

**UNIT-IV**

7. Draw a state diagram for a sequence checker, whose output will be '1' whenever the sequence 1011 is detected. Develop a one-hot design for the same sequence checker. 12M

**OR**

8. a) What are the features of the extended Petri Nets used for parallel controllers? 6M  
 b) Explain the Micro-programming linked state machine with an example. 6M

**UNIT-V**

9. a) Explain FSM architectures centered around non-registered PLDs. 6M  
 b) With suitable example, explain system level design by considering controller, data path. 6M

**OR**

10. a) Explain the design approach of state machines centered around shift registers. 6M  
 b) With an example explain about One-Hot design method using ASMs. 6M

\*\*\*

Hall Ticket Number :

R14

**Code: 4PB311**

*M.Tech. I Semester Regular & Supplementary Examinations Feb/Mar 2016*

**Embedded System Concepts**

*(Common to DECS, Embedded Systems, VLSISD)*

Max. Marks: 60

Time: 3 Hours

Answer all five units by choosing one question from each unit ( 5 x 12 = 60 Marks )

\*\*\*\*\*

**UNIT-I**

1. Discuss the following in details
- i) Characteristics and constraints of embedded systems
  - ii) Classifications of embedded systems
- 12M

**OR**

2. Explain about significance of each hardware unit present in embedded design
- 12M

**UNIT-II**

3. a) Compare Harvard and Princeton memory organizations. 4M  
b) Why should a program be divided into functions (routines or modules) and each placed in different memory blocks or segments 8M

**OR**

4. What are the different memories, input and output devices used In embedded systems? How will you interface these input and output devices in embedded systems 12M

**UNIT-III**

5. What is meant by scheduling? How do schedule the tasks with different algorithms 12M

**OR**

6. Explain about different buses used in parallel communication between networked devices 12M

**UNIT-IV**

7. What is meant by co-design? Explain design & co-design issues in system development process 12M

**OR**

8. Discuss different design methodologies for embedded system. 12M

**UNIT-V**

9. Describe the classes, the objects which are used in writing codes for saving an image file in a digital camera? 12M

**OR**

10. How do you design an automatic chocolate vending machine? Explain clearly. 12M

\*\*\*